



EE281

First Order Circuits

Dr. M. Mert ANKARALI


First-Order Circuits

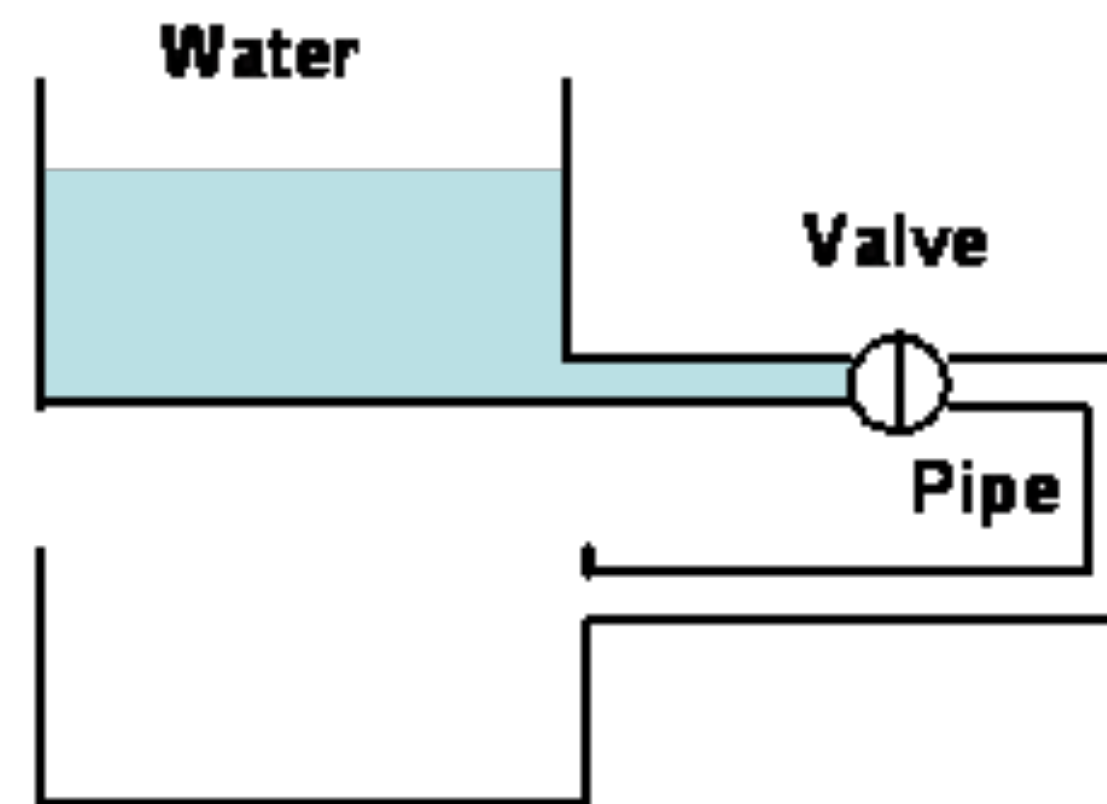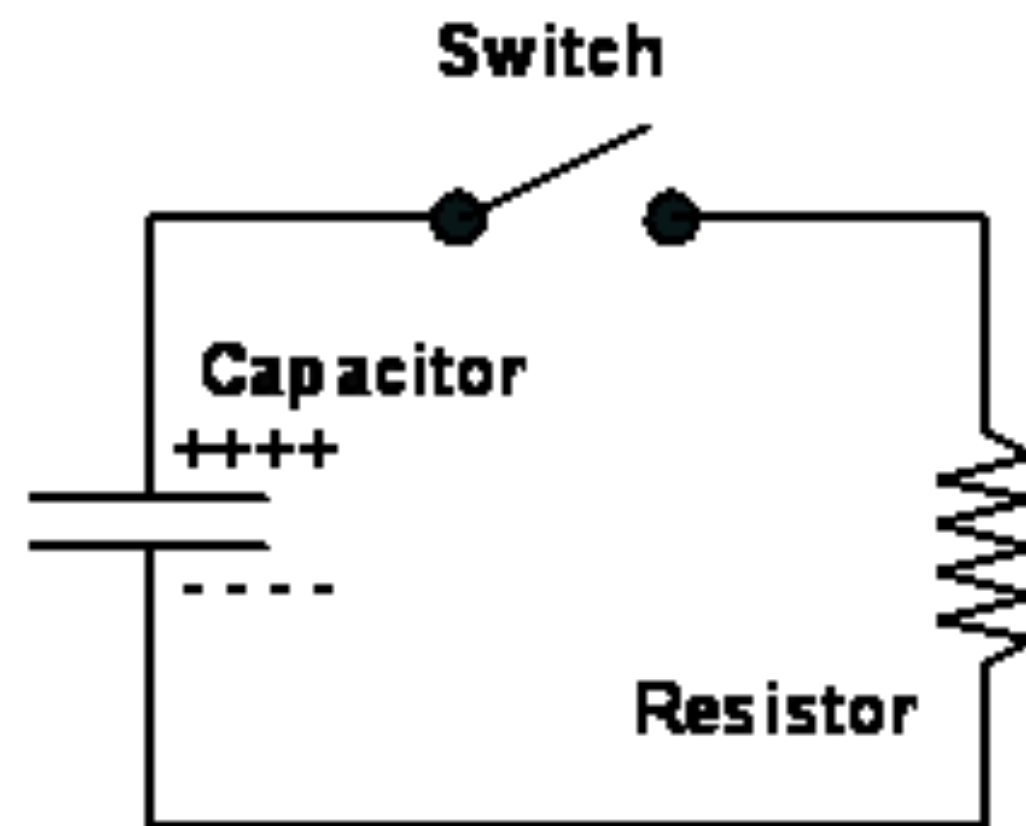- Contains one independent energy storage element (capacitor or inductor)
- Can be described using a first-order differential equation
- Two types: RC or RL circuits
- Electrical RC Circuit and Hydraulic Analogy




RC Circuits

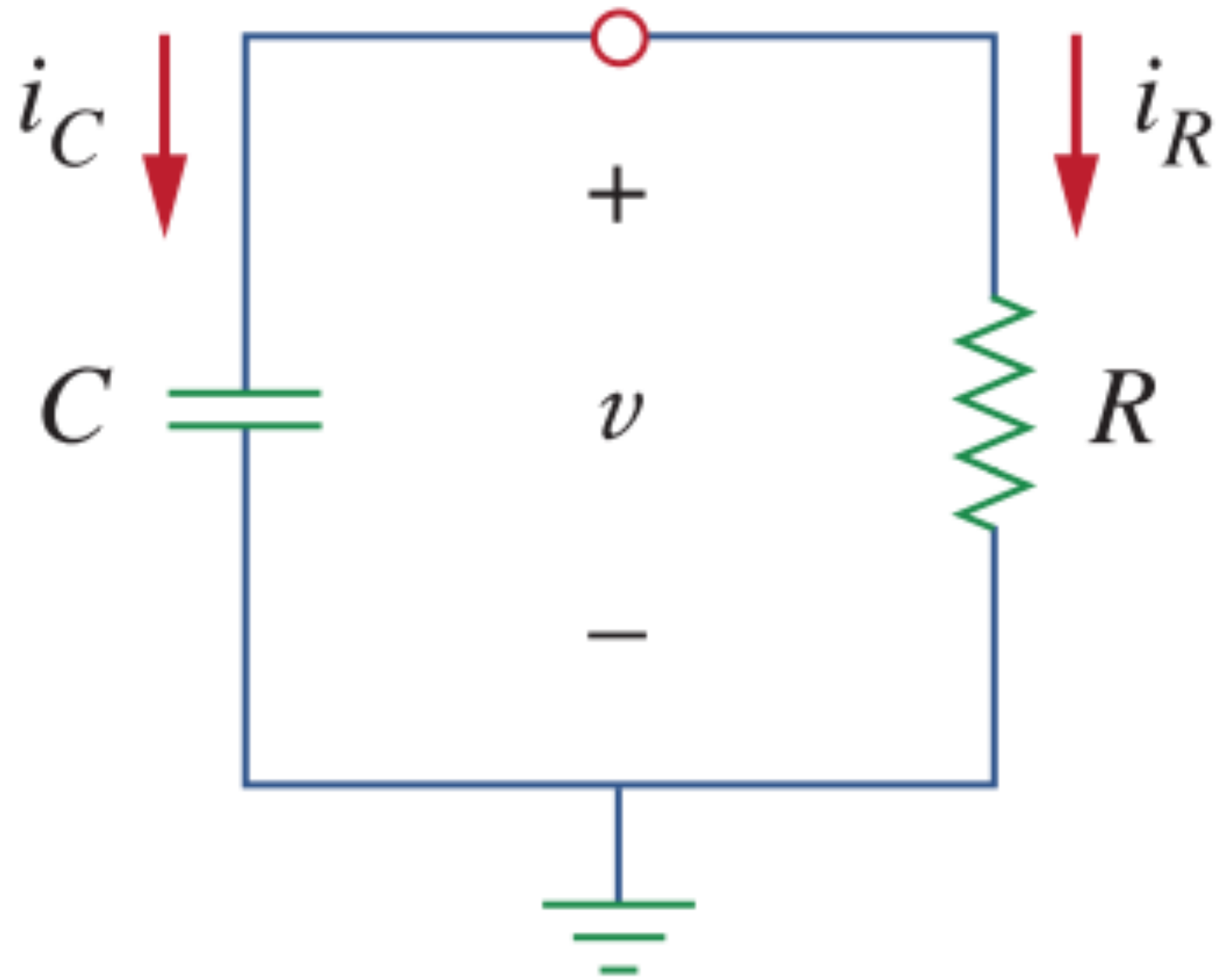- Assume that at $t=0$, the capacitor voltage is equal to V_0




RC Circuits

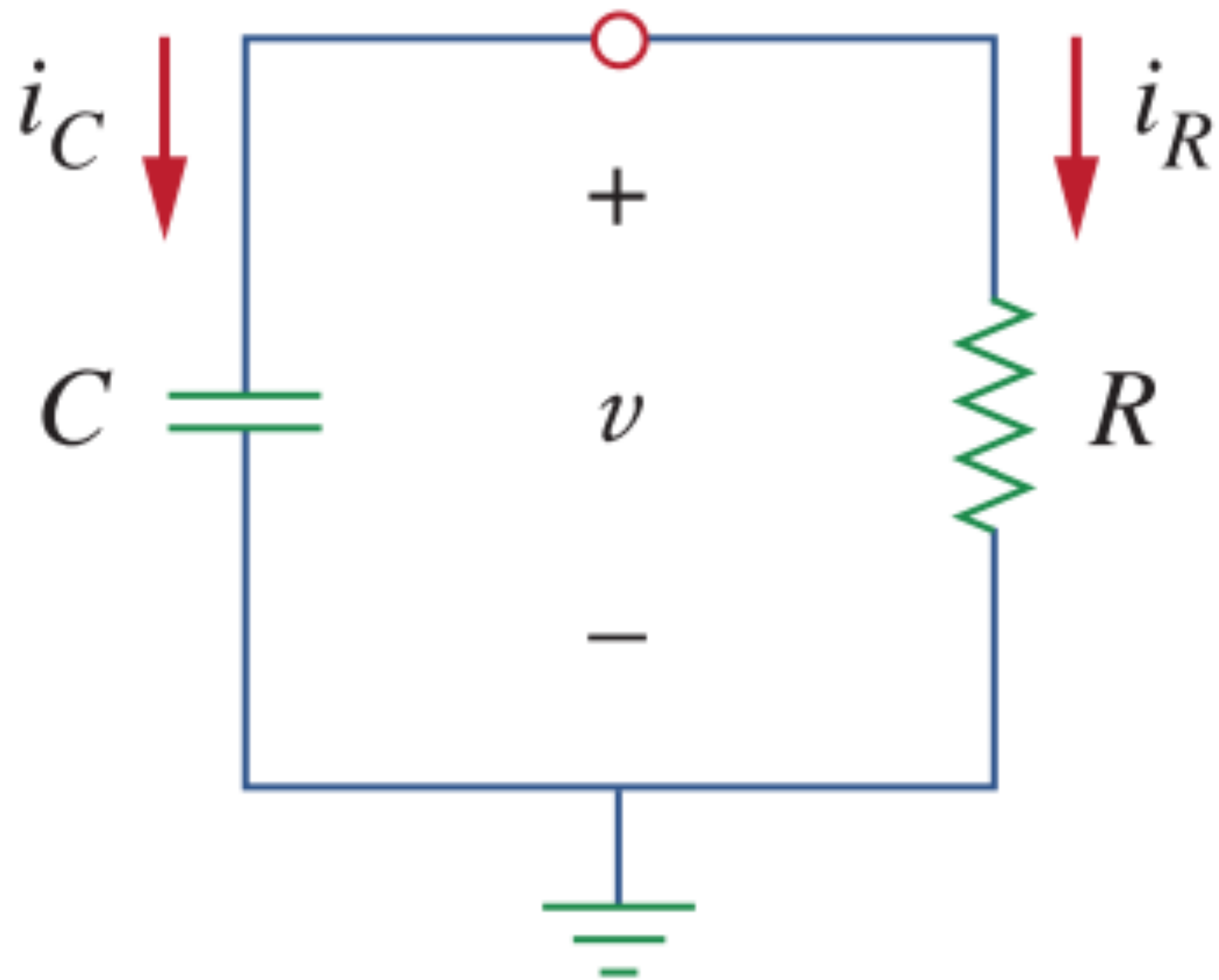- Assume that at $t=0$, the capacitor voltage is equal to V_0



RC Circuits

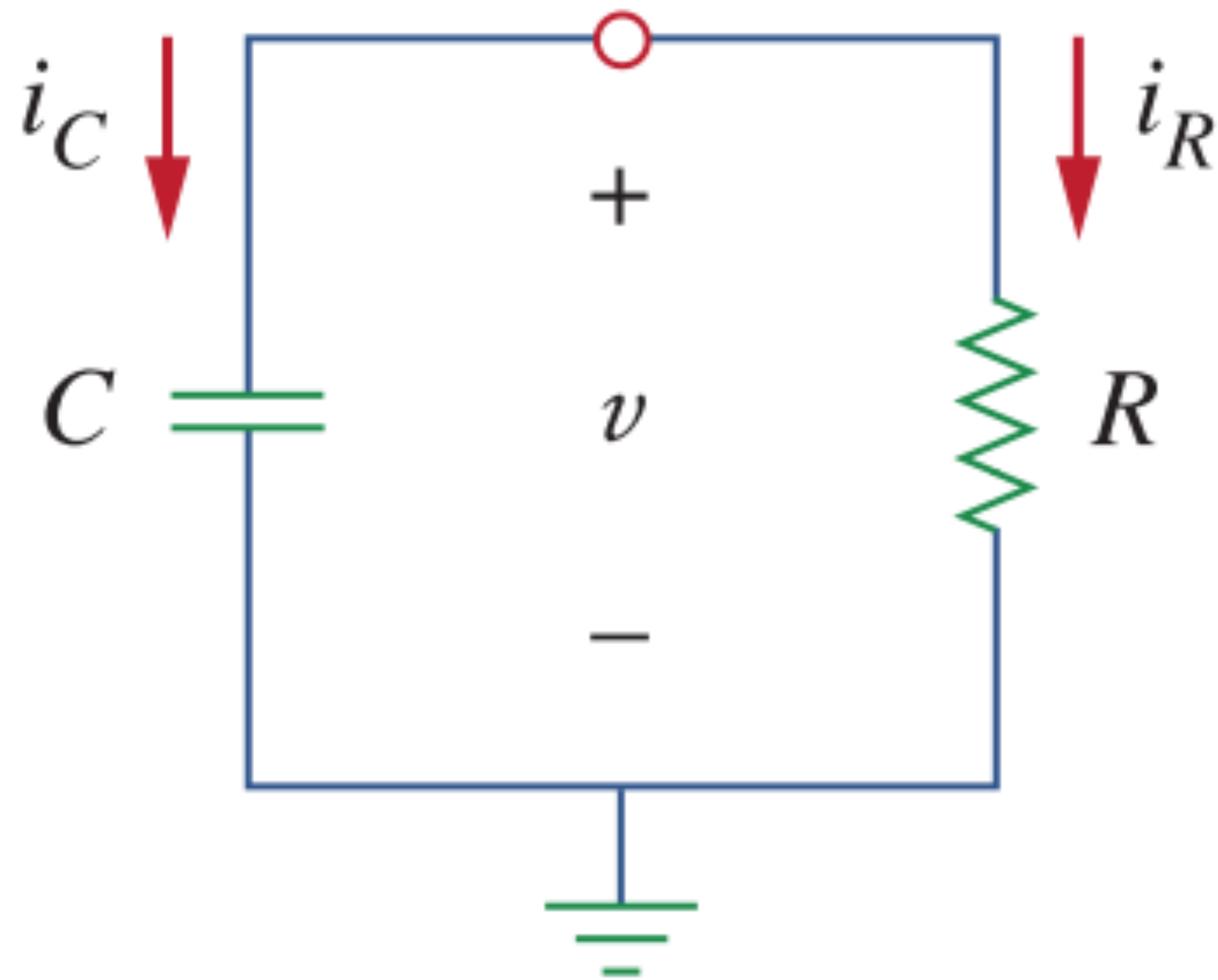- Assume that at $t=0$, the capacitor voltage is equal to V_0




$$V_0(t) = V_0 e^{\frac{-t}{RC}} = V_0 e^{\frac{-t}{\tau}}$$

τ : Time Constant


Exponential Decay

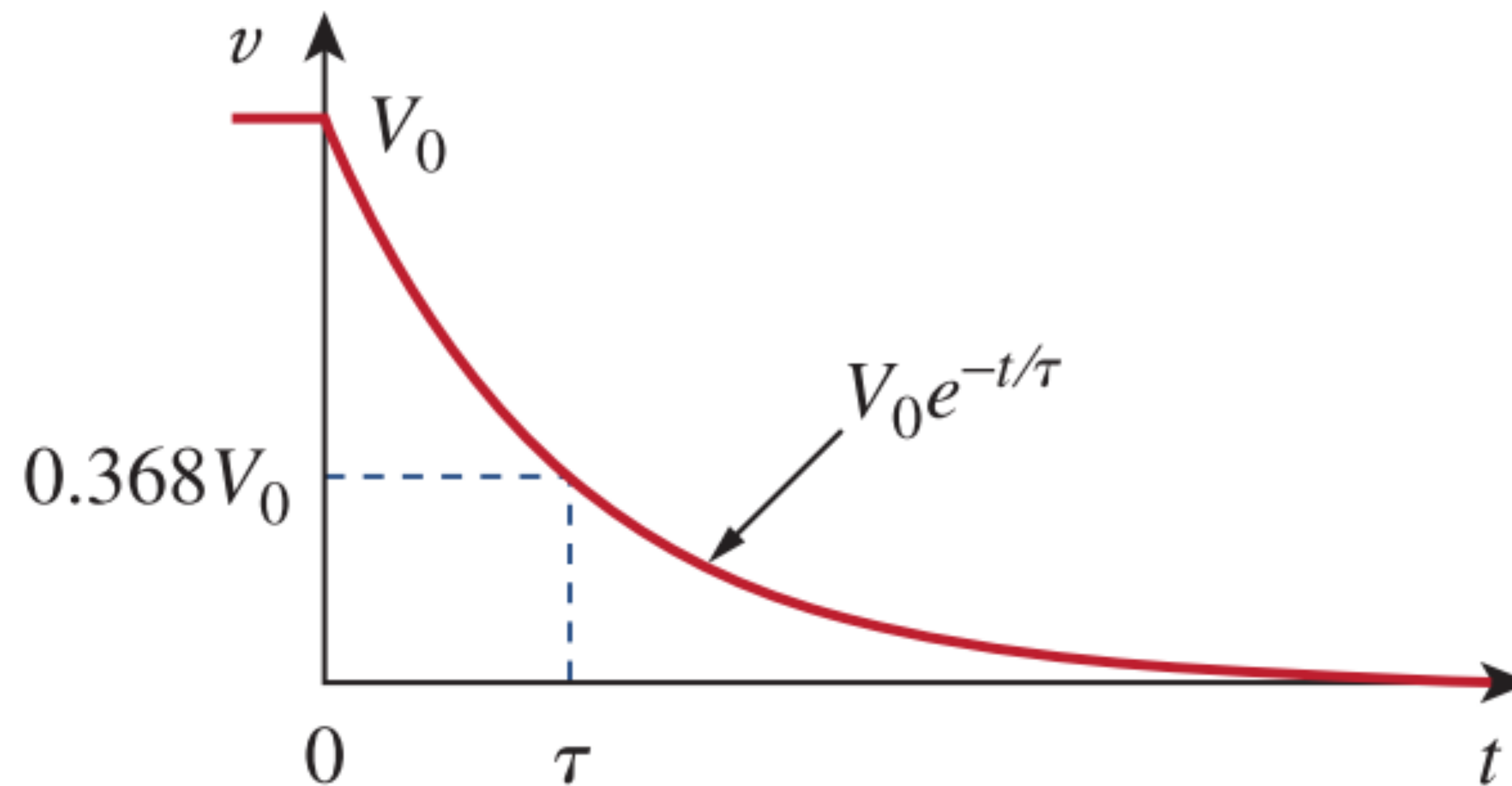- Chemical Reactions, Fluid Dynamics, Heat Transfer, Atmospheric Pressure, Radioactivity



RC Example

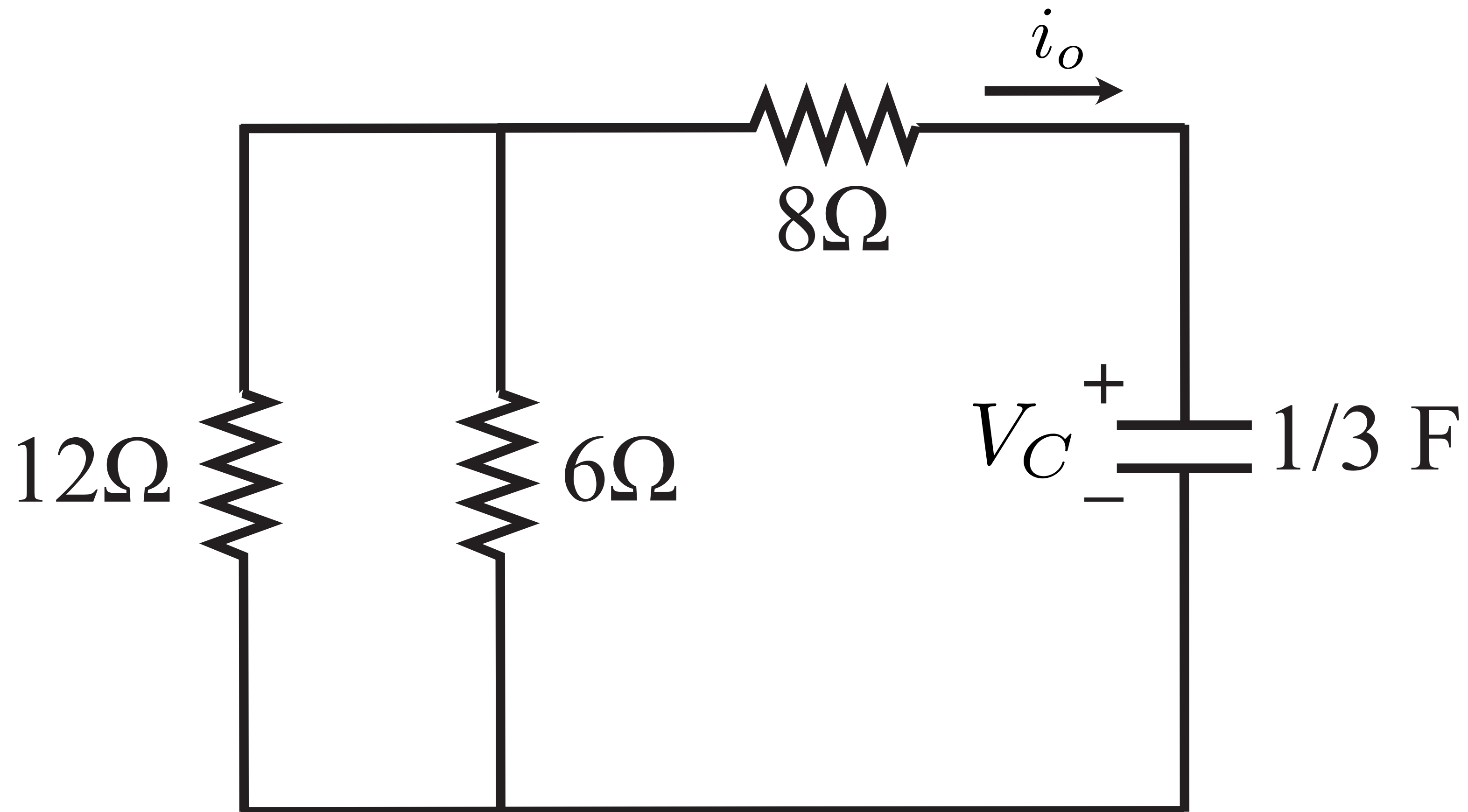
- Initial voltage of the capacitor is 60 V, then determine V_c & i_o



RC Example


$$R_{eq} = \left[8 + \left(\frac{12 \cdot 6}{12 + 6} \right)^{-1} \right] \Omega = 12 \Omega$$

$$\tau = R_{eq} C = 4 \text{ s}$$

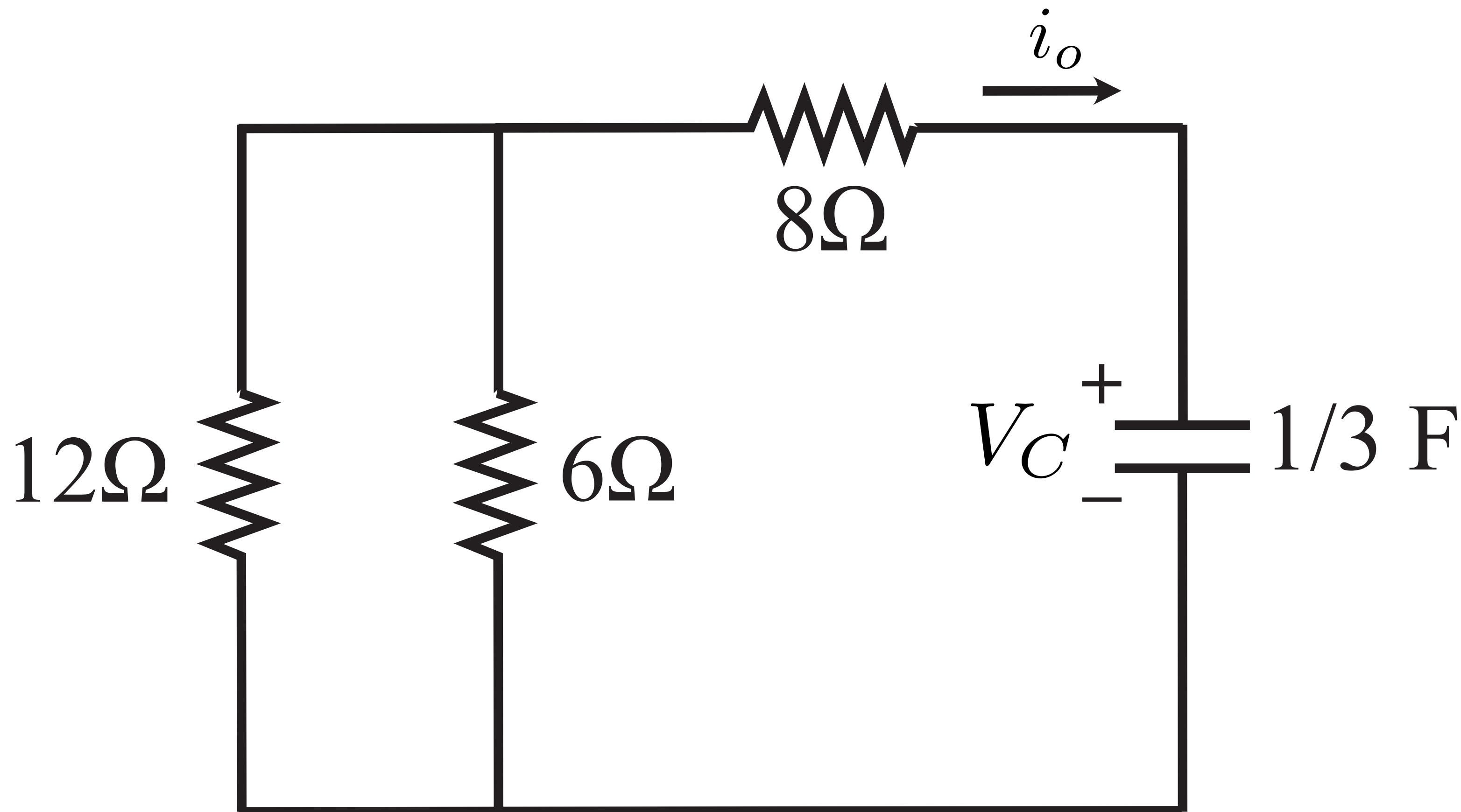

$$R_{eq} = \left[8 + \left(\frac{12 \cdot 6}{12 + 6} \right)^{-1} \right] \Omega = 12 \Omega$$

$$\tau = R_{eq} C = 4 \text{ s}$$

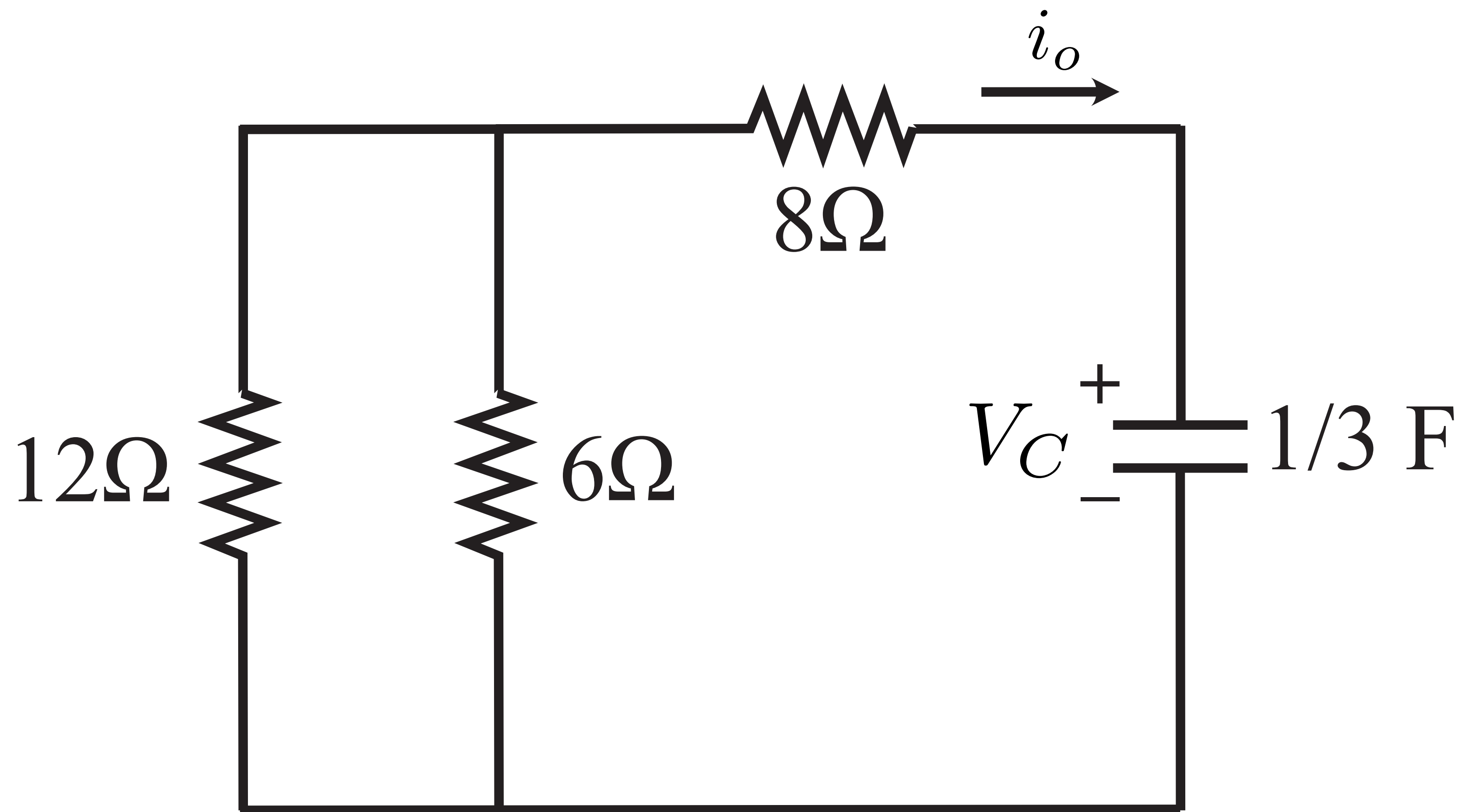


$$R_{eq} = \left[8 + \left(\frac{12 \cdot 6}{12 + 6} \right)^{-1} \right] \Omega = 12 \Omega$$

$$\tau = R_{eq} C = 4 \text{ s}$$


$$V_c(t) = 60 e^{-t/4}$$

$$i_o(t) = -5 e^{-t/4} \text{ A}$$

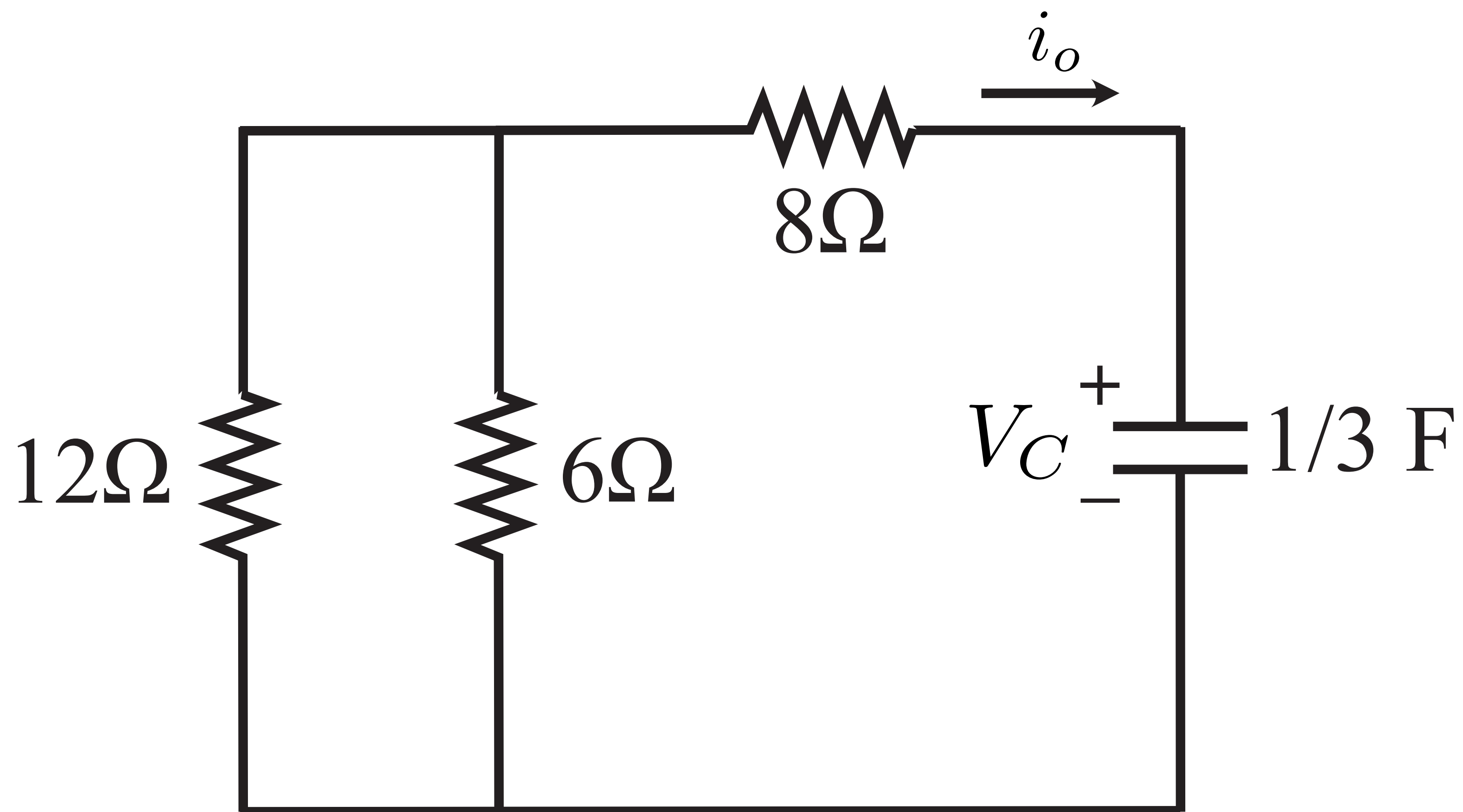


RL Circuits

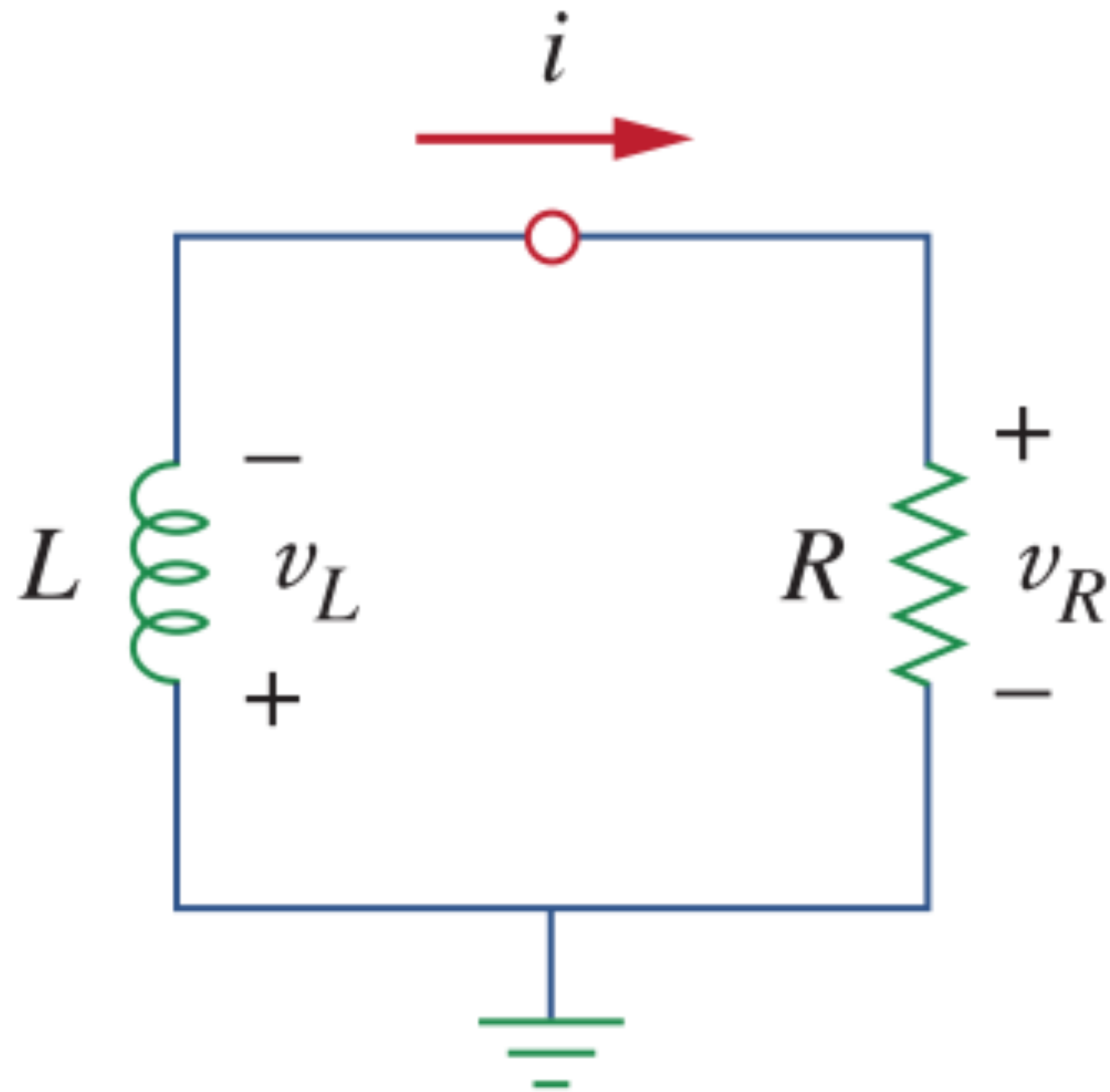- Assume that at $t=0$, the inductor current is equal to I_0



RL Circuits

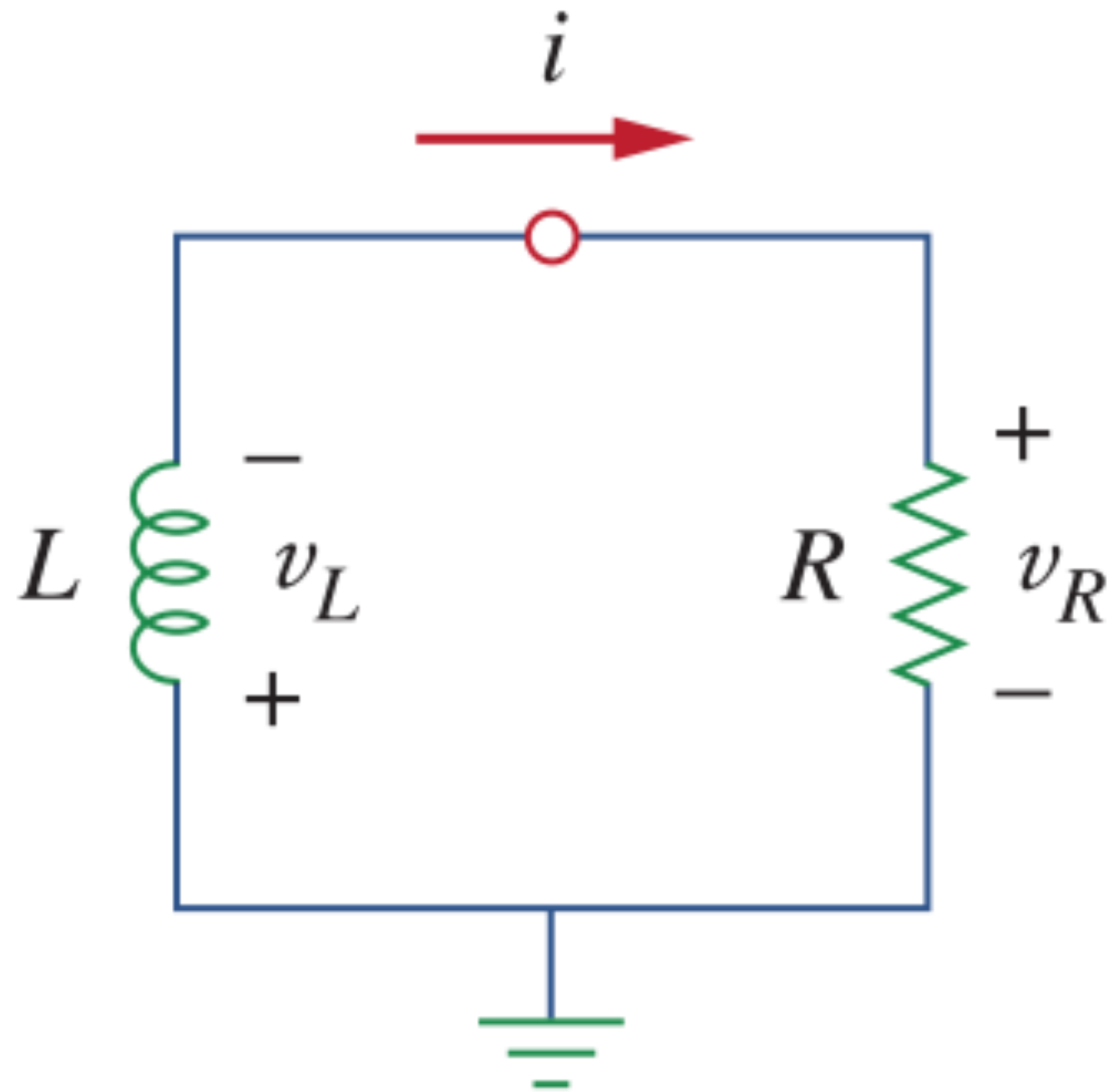
- Assume that at $t=0$, the inductor current is equal to I_0



$$\tau = L/R$$


$$I_0(t) = I_0 e^{\frac{-t}{\tau}} = I_0 e^{\frac{-R}{L}t}$$

RL Circuits

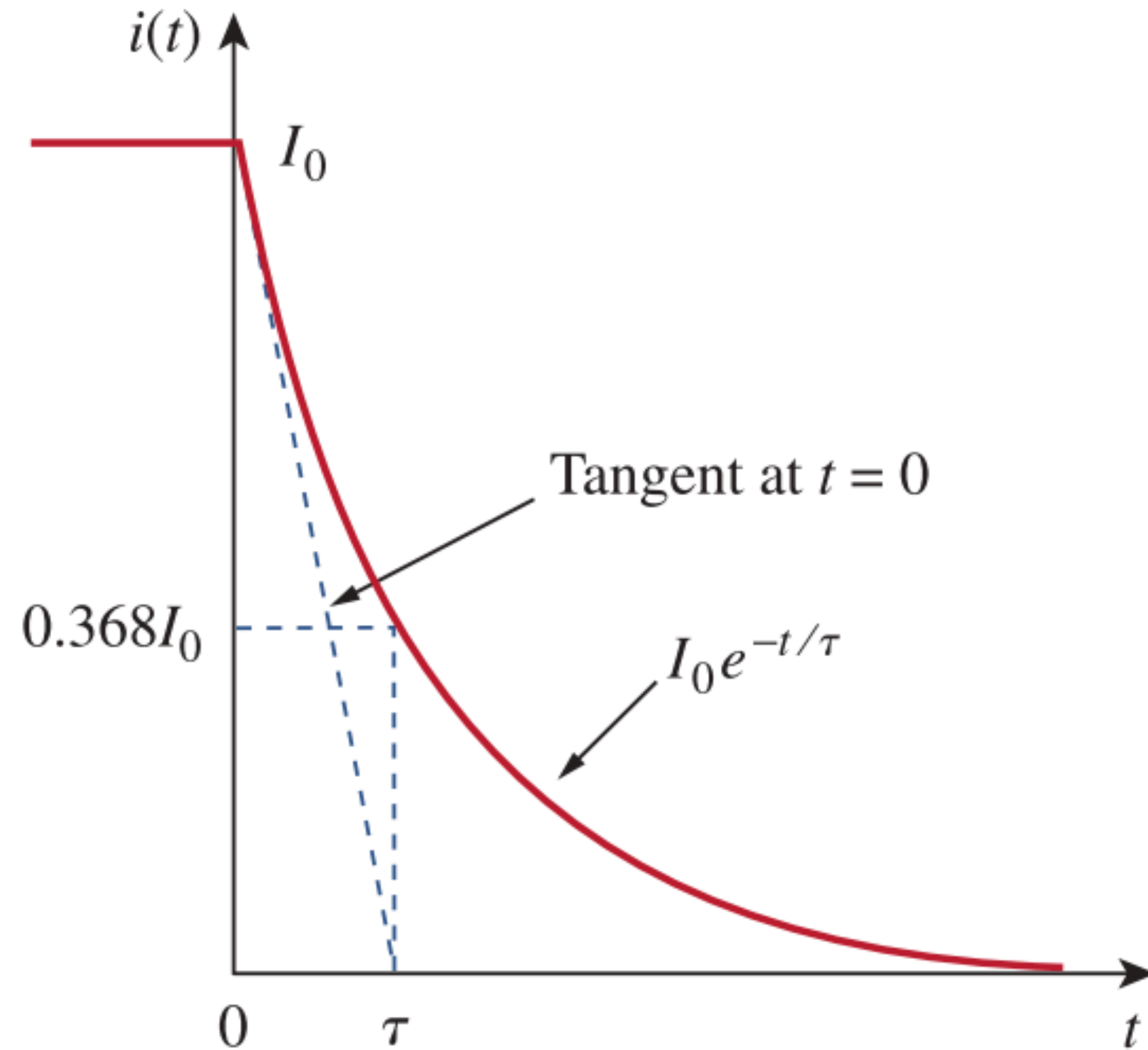


RL Example

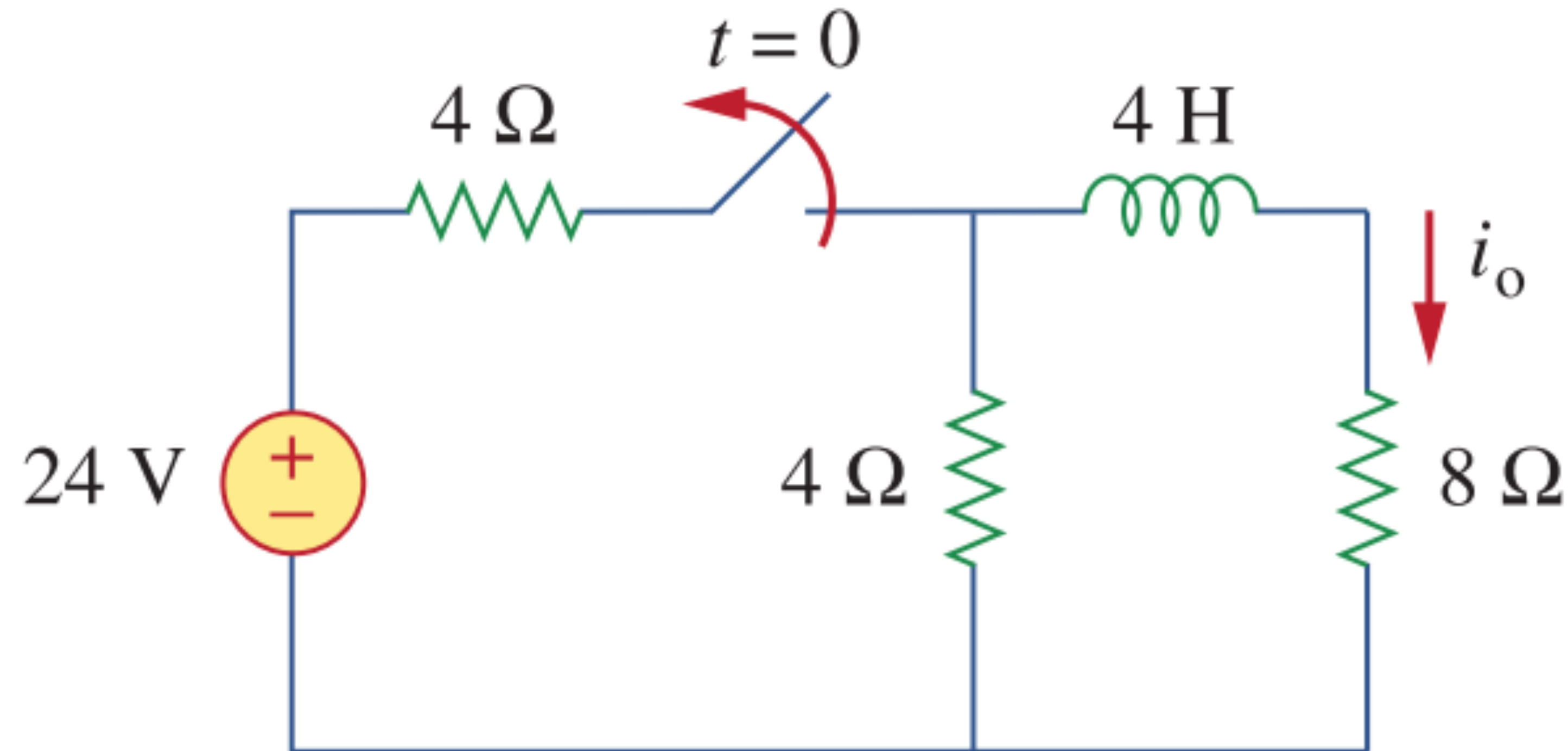
- Assume that at $t < 0$ the switch is in closed condition and the circuit had reached steady-state conditions
- At $t = 0$, we open the switch. Compute $i_o(t)$




RL Example

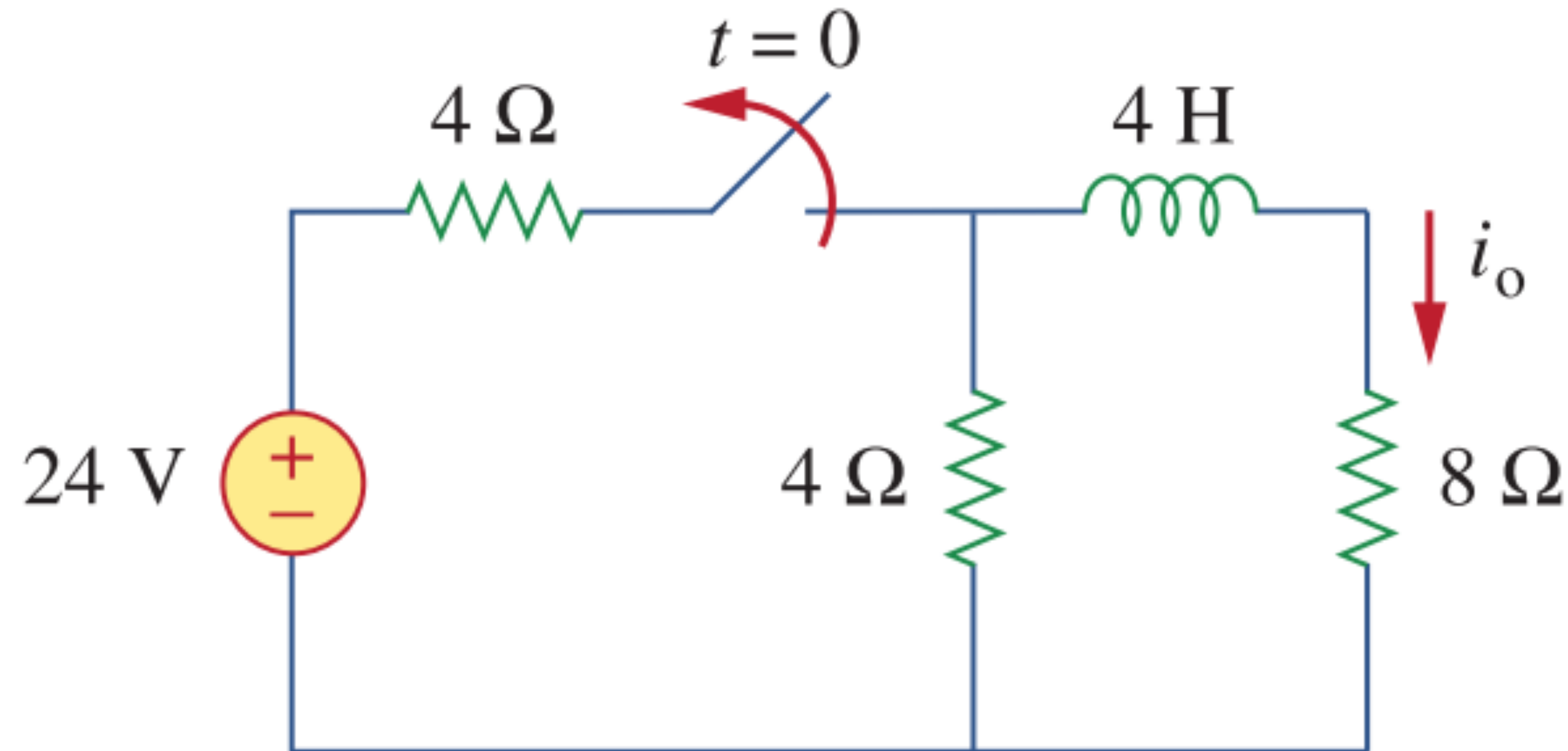- Assume that at $t < 0$ the switch is in closed condition and the circuit had reached steady-state conditions
- At $t = 0$, we close the switch. Compute $i_o(t)$




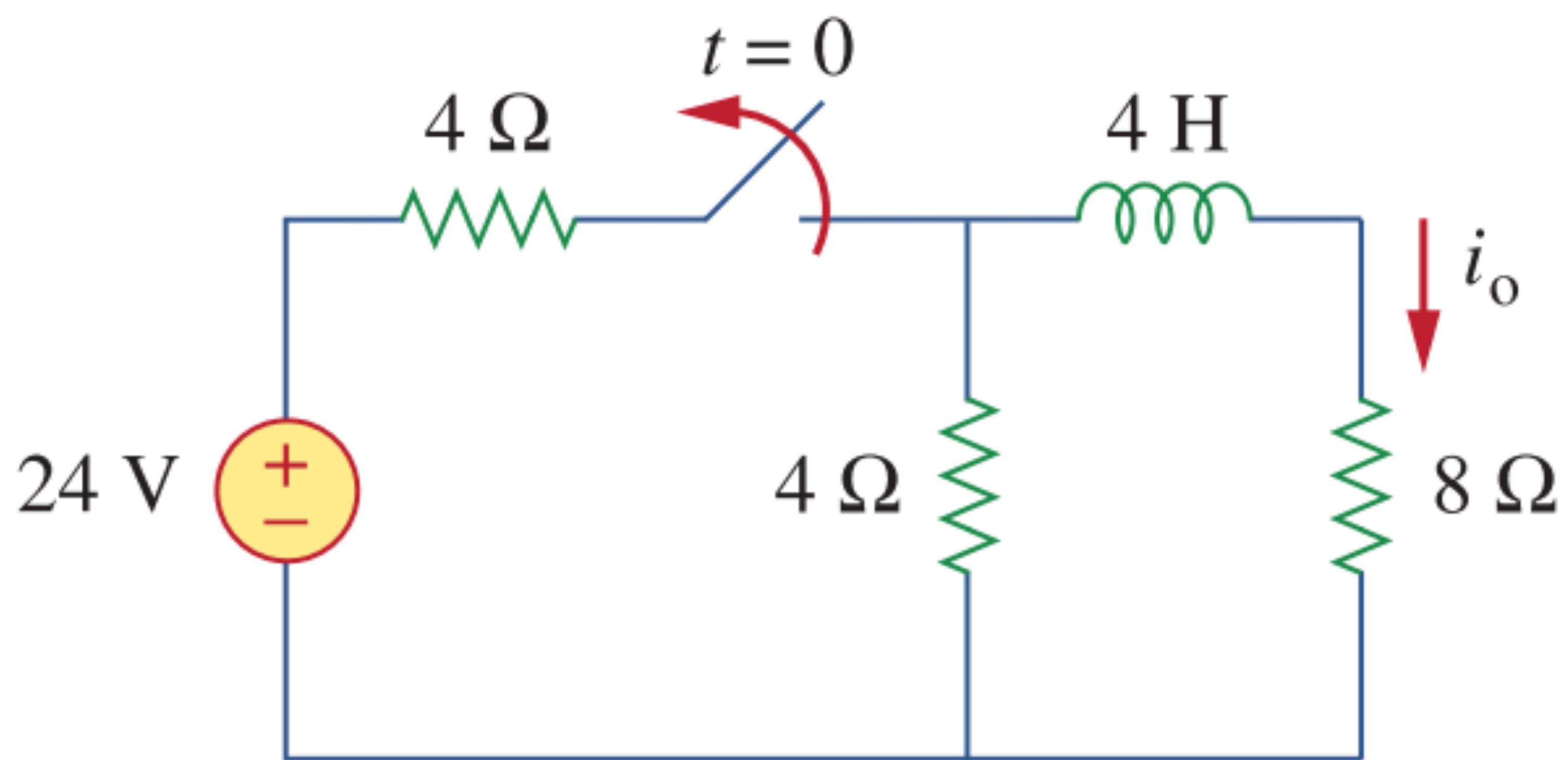


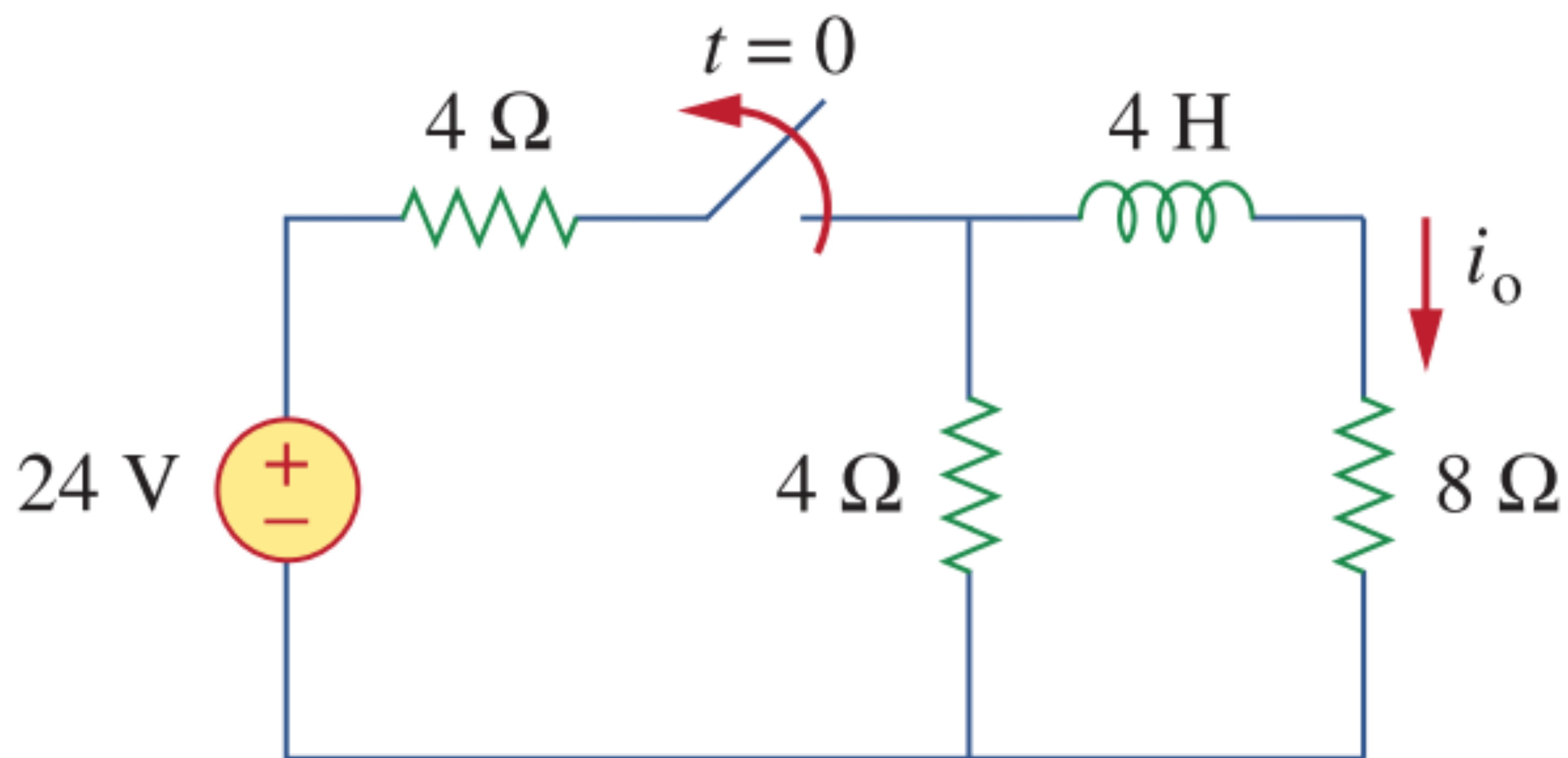


$$i_o(t) = 1.2e^{-3t} A$$

RL Example 2

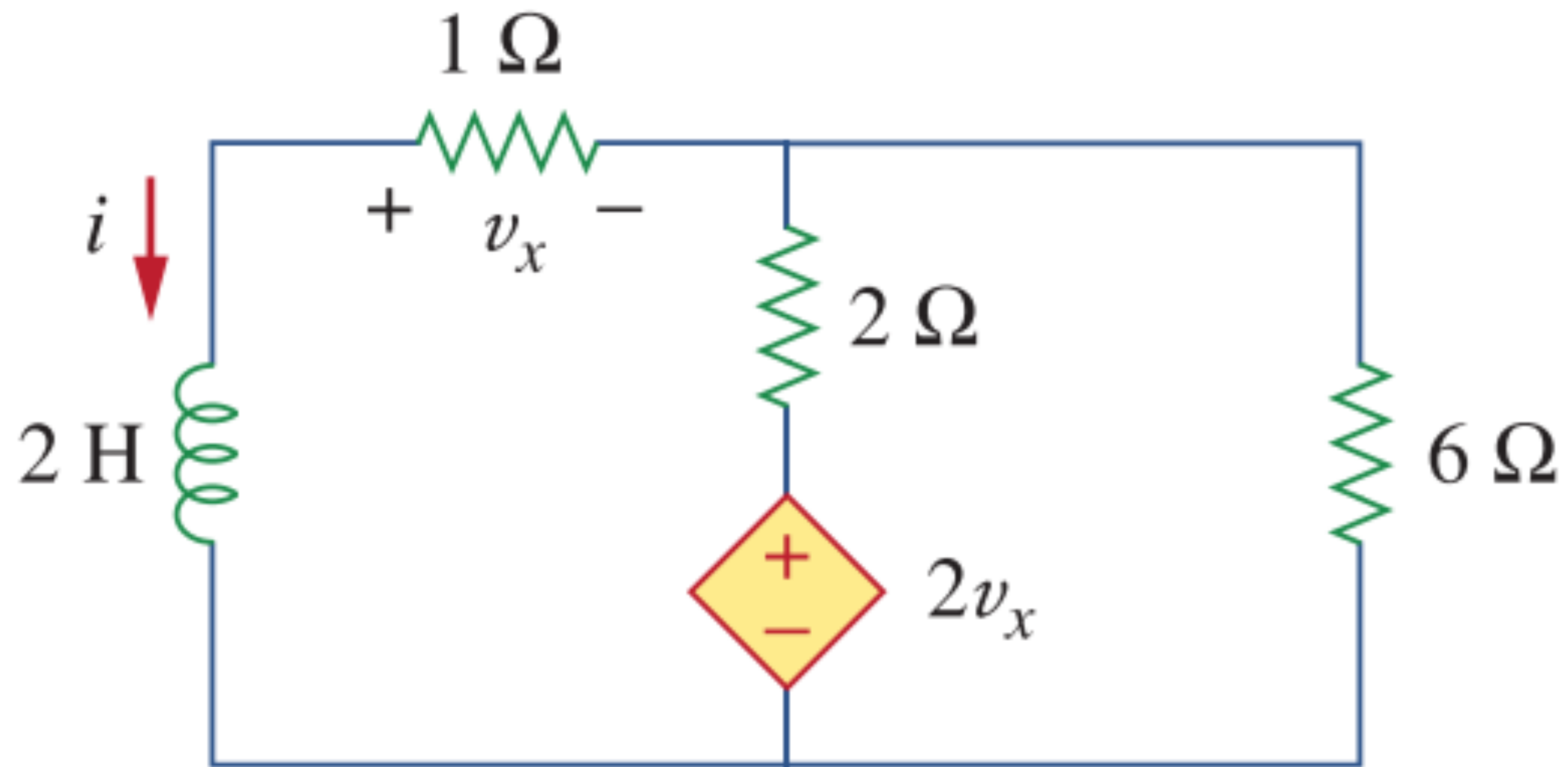

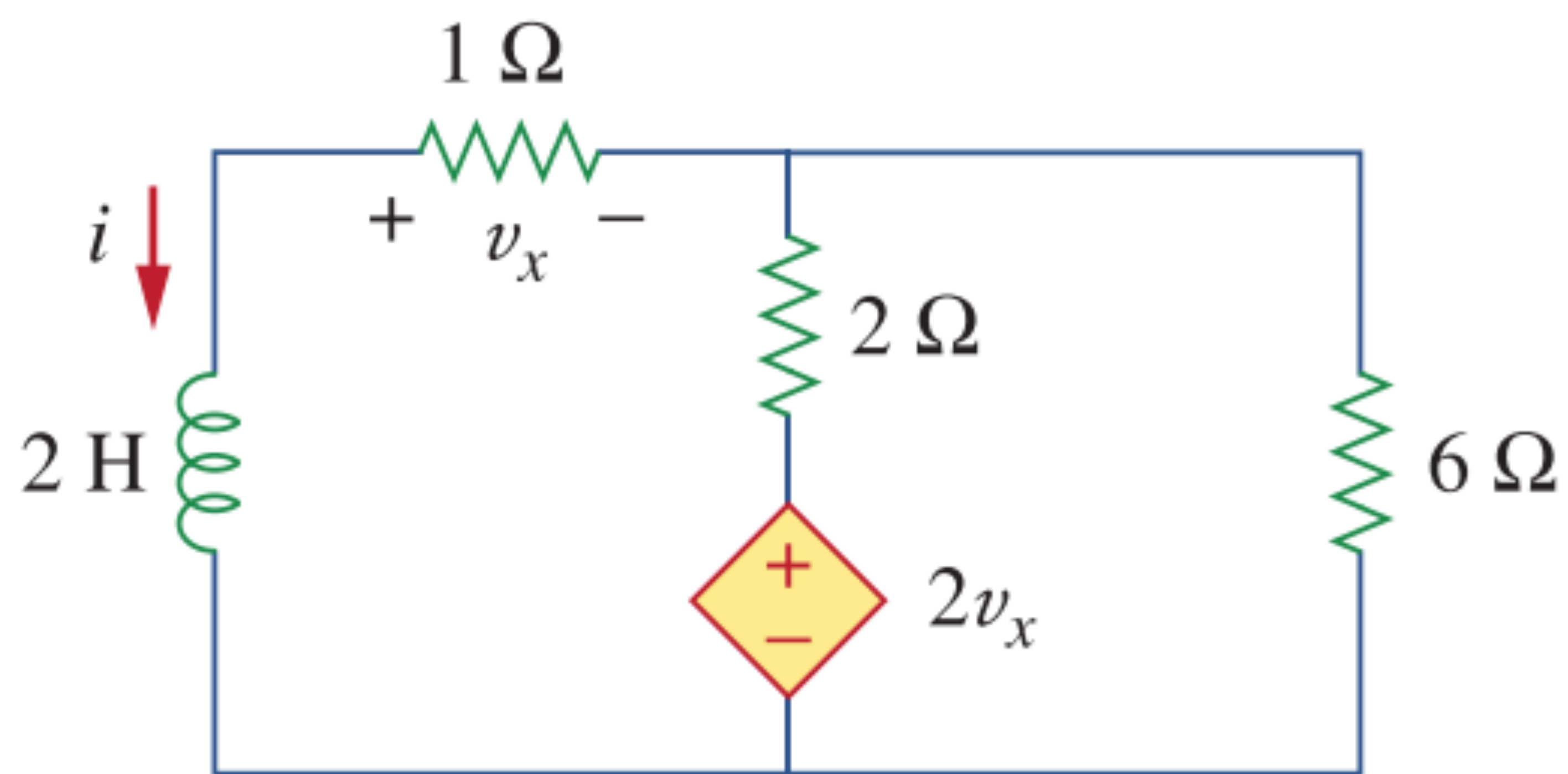

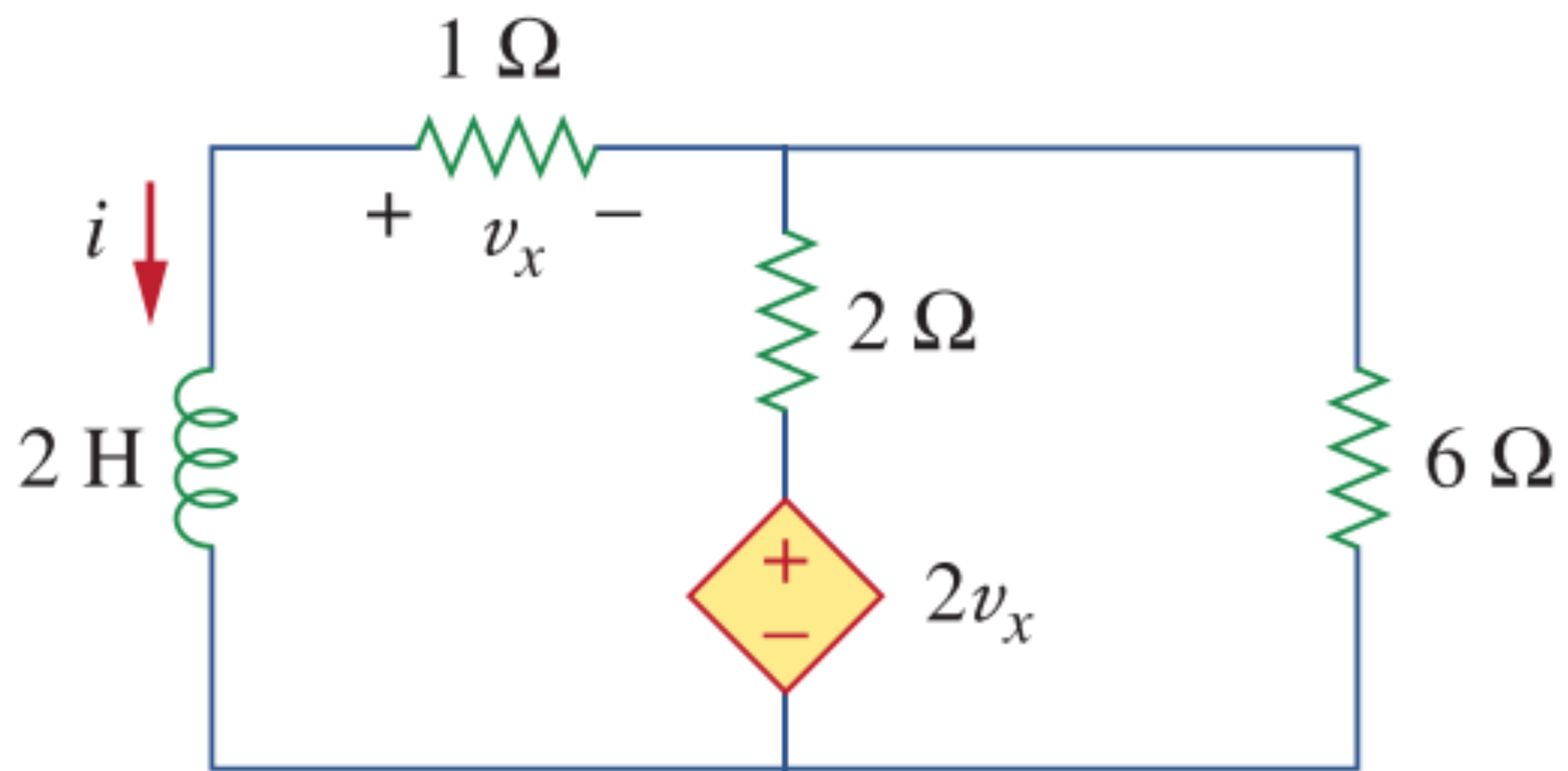

$$\tau = 1/2s$$