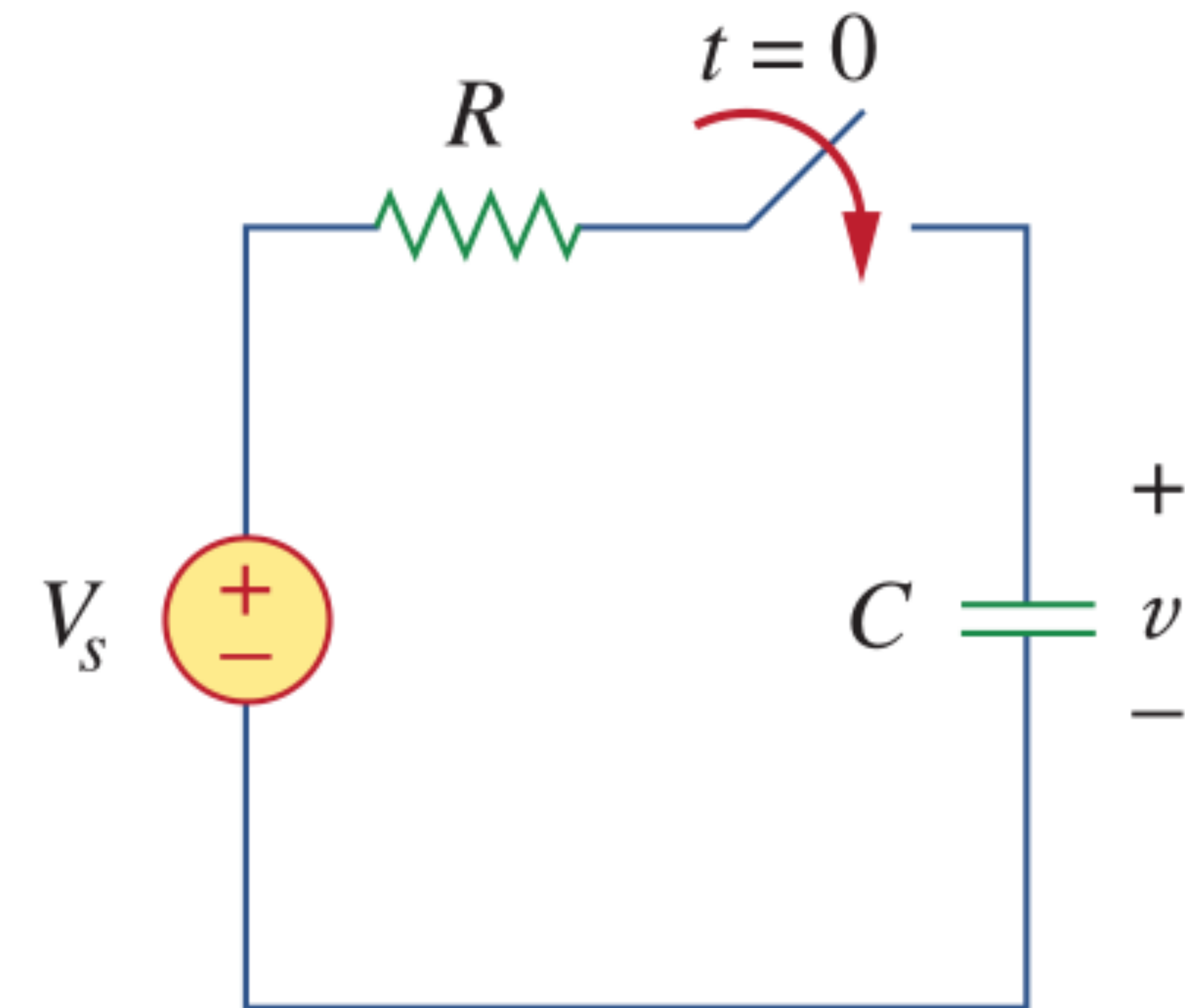


Step Response - RC Circuits



- Assume that at $t=0$, the capacitor voltage is equal to 0V



Step Response - RC Circuits


- Assume that at $t=0$, the capacitor voltage is equal to 0V
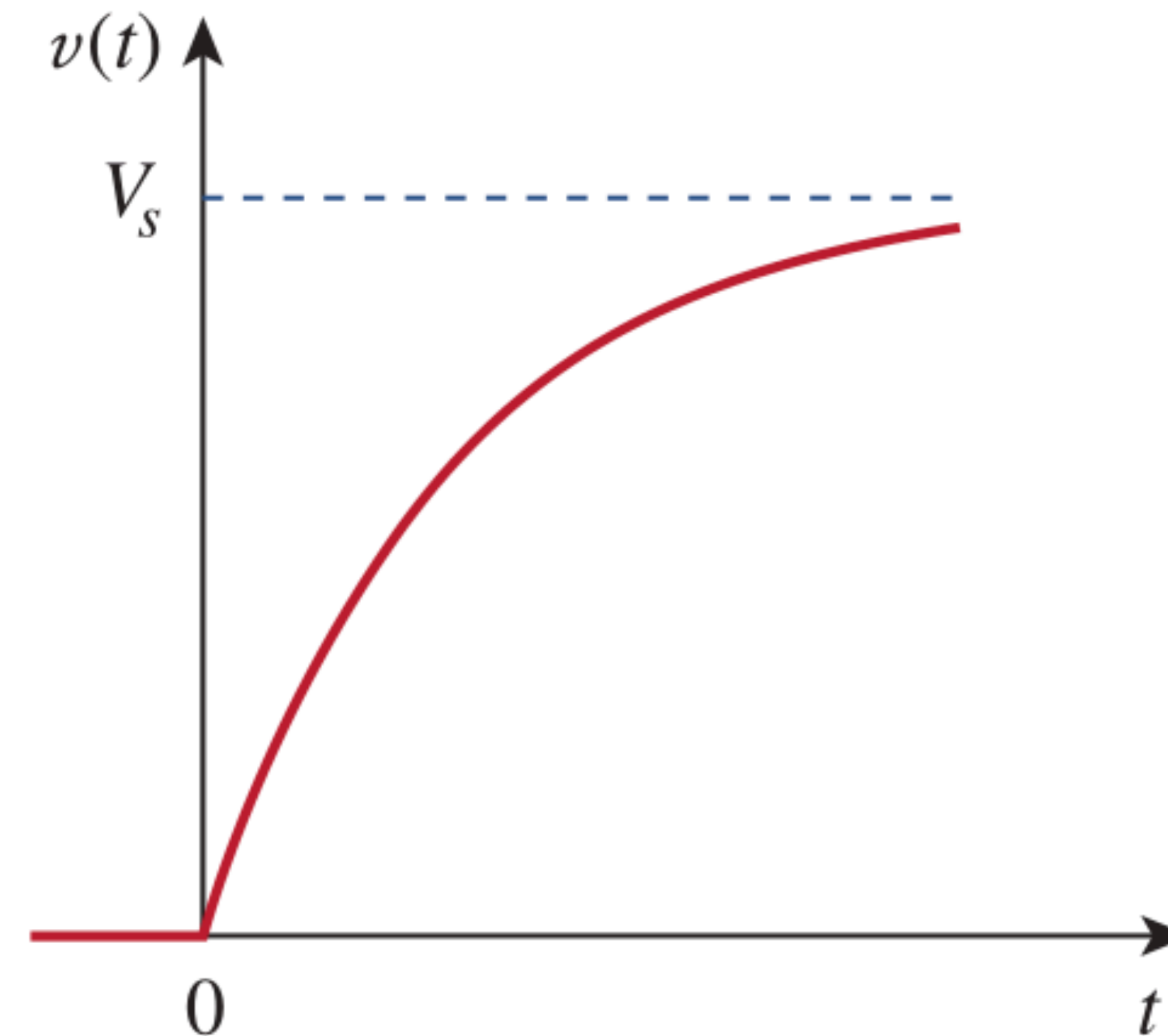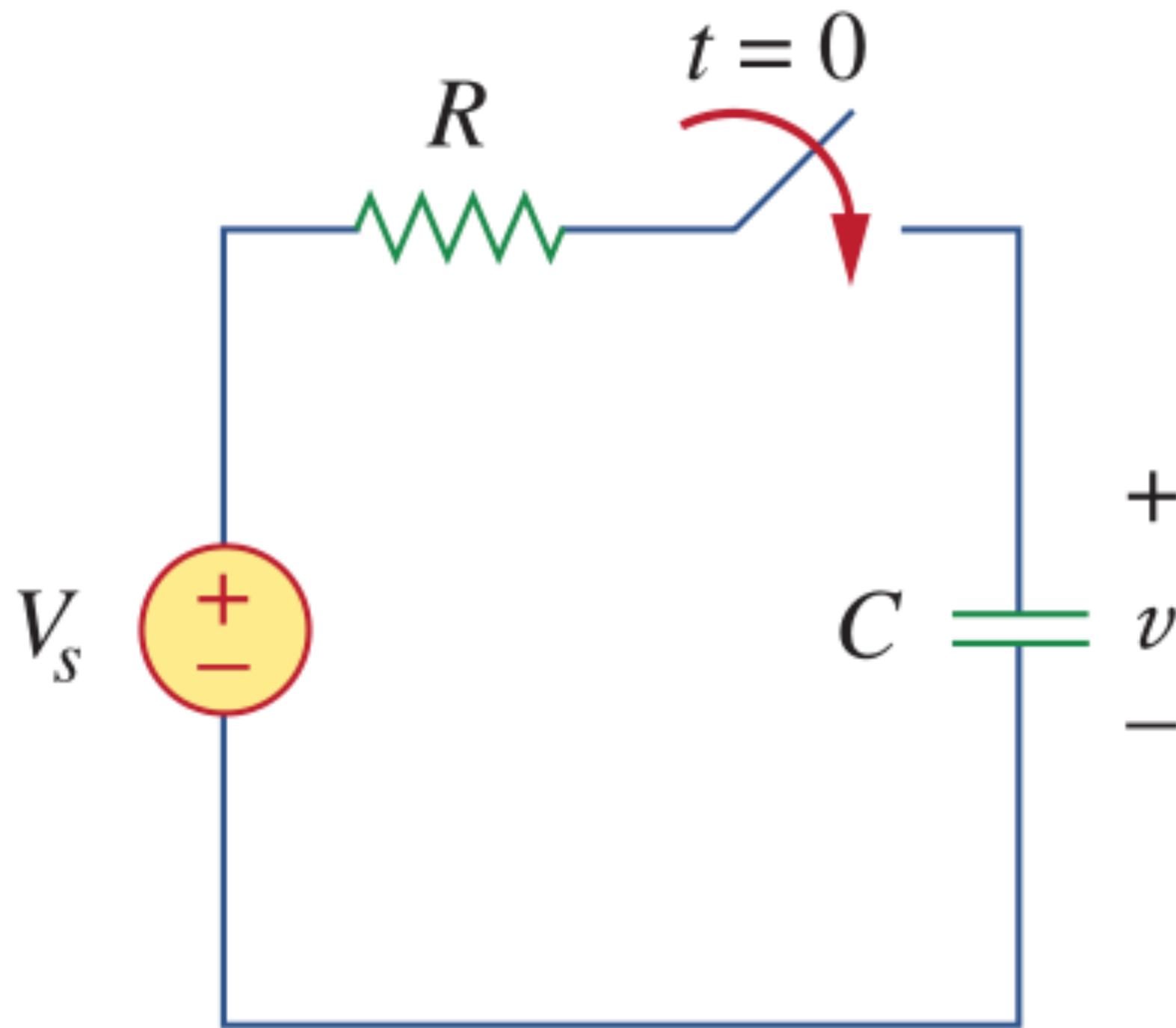
$$v(t) = V_s \left(1 - e^{\frac{-t}{RC}} \right) = V_\infty \left(1 - e^{\frac{-t}{\tau}} \right)$$



Step Response - RC Circuits


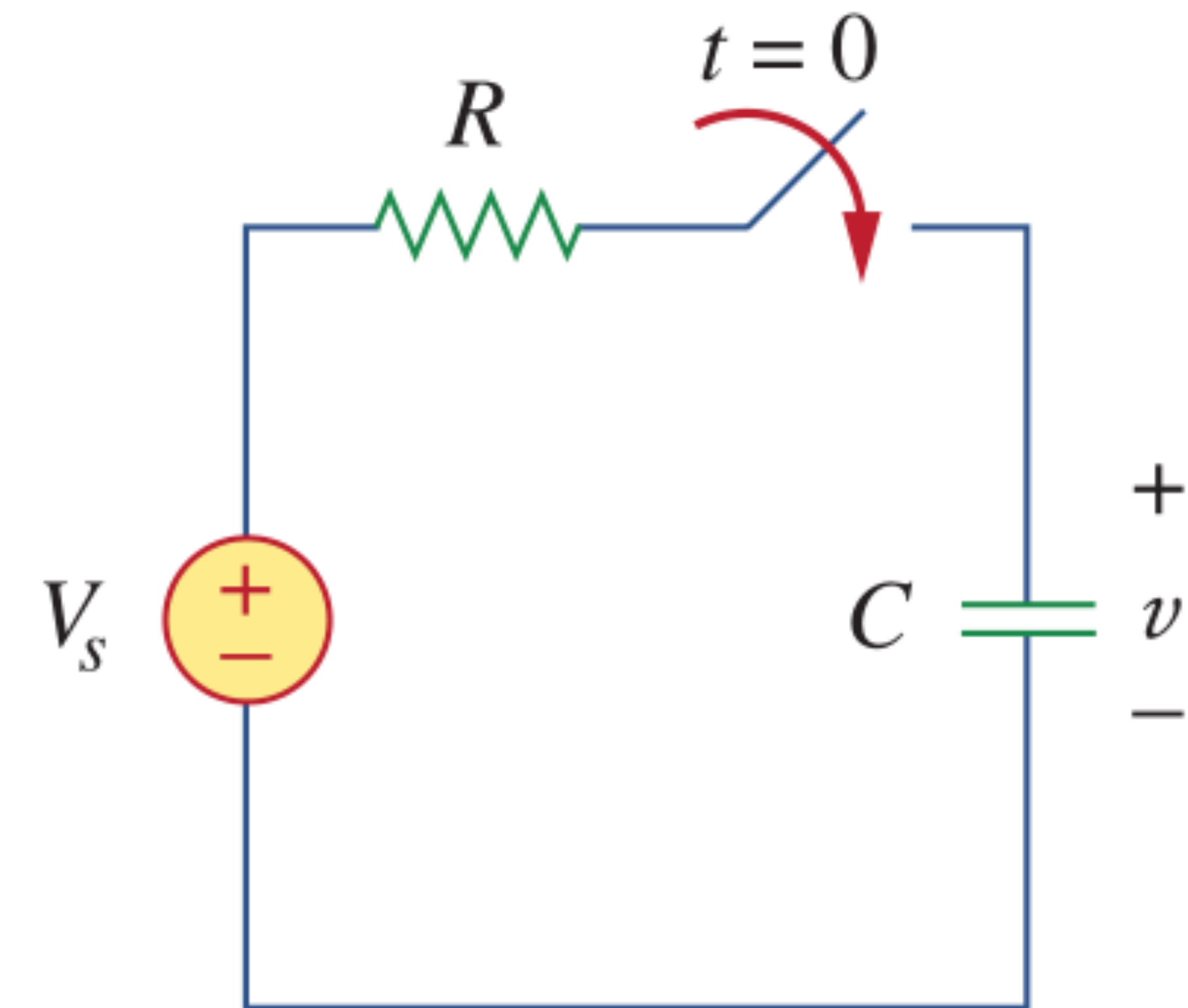
- Assume that at $t=0$, the capacitor voltage is equal to V_o



Step Response - RC Circuits


- Assume that at $t=0$, the capacitor voltage is equal to V_0

$$\begin{aligned} V_c(t) &= V_s + (V_0 - V_s)e^{-t/\tau} \\ &= V_\infty + (V_0 - V_\infty)e^{\frac{-t}{RC}} \end{aligned}$$

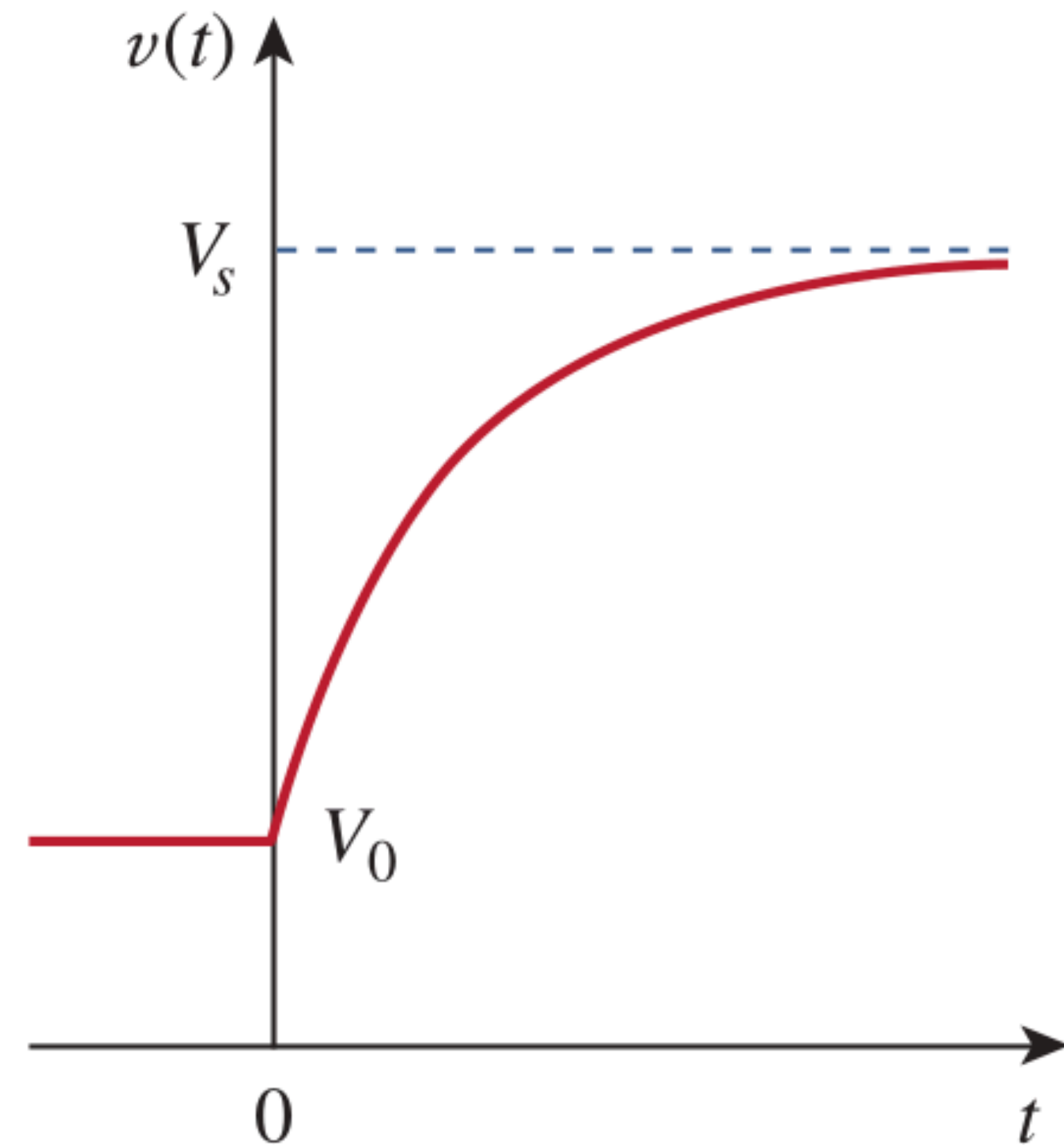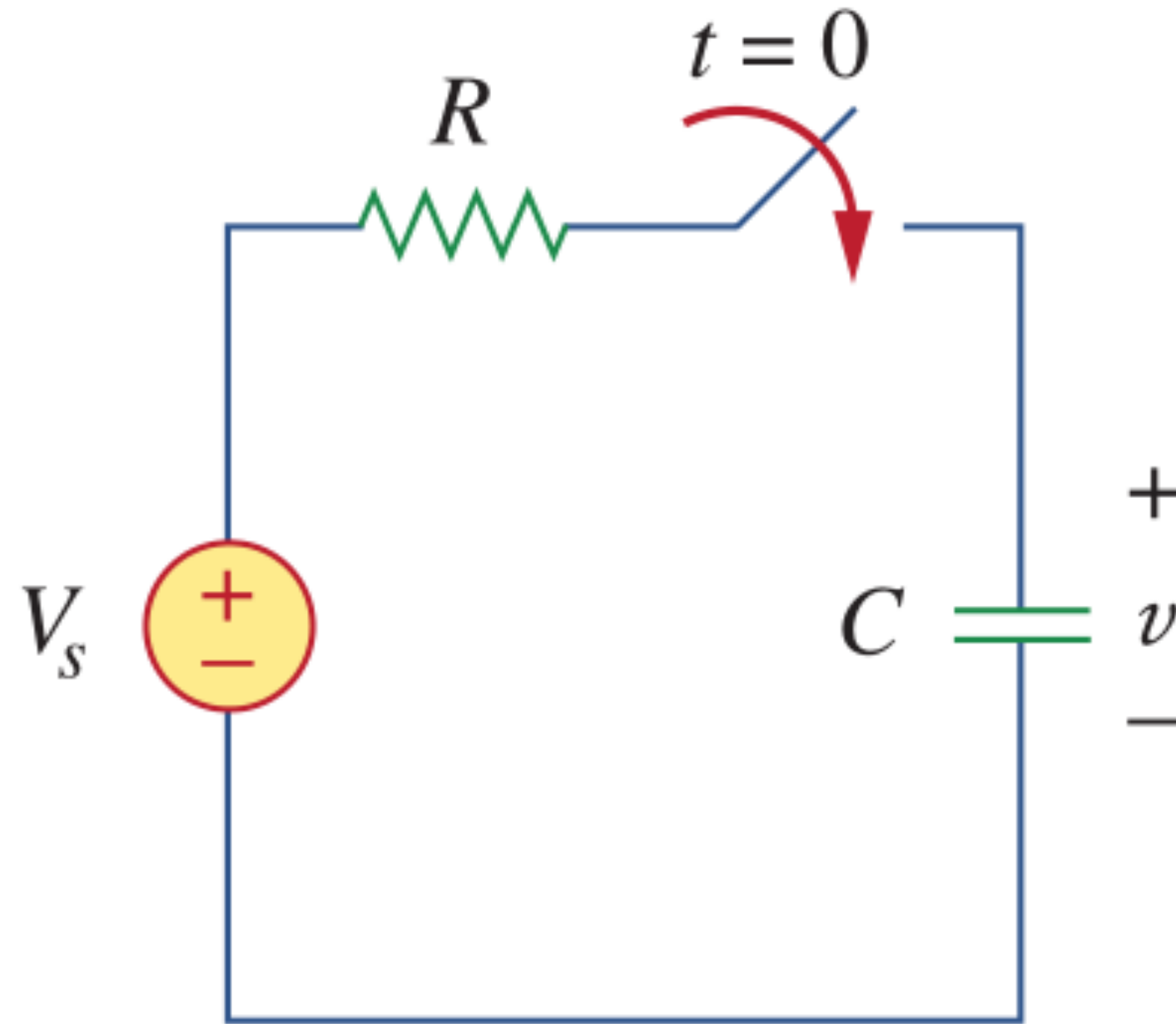


Example 1 - Step-Response in RC Circuits

- Determine $v(t)$

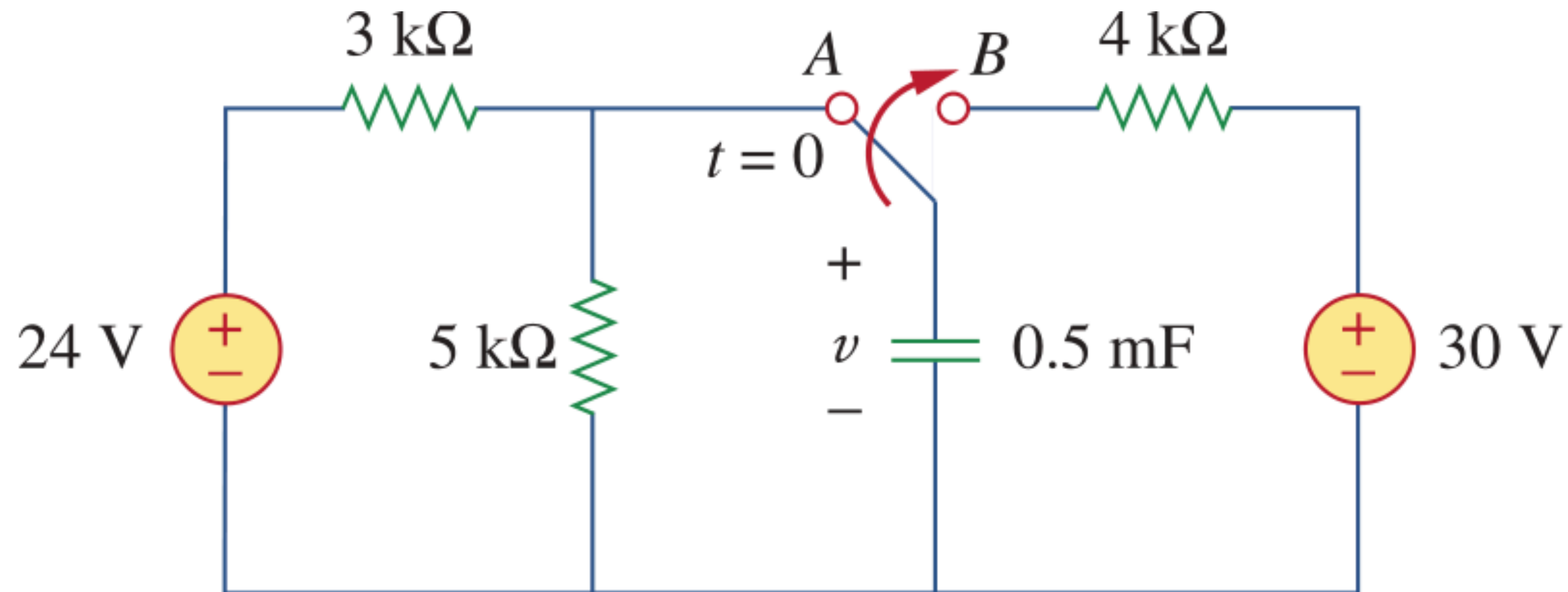

Example 1 - Step-Response in RC Circuits

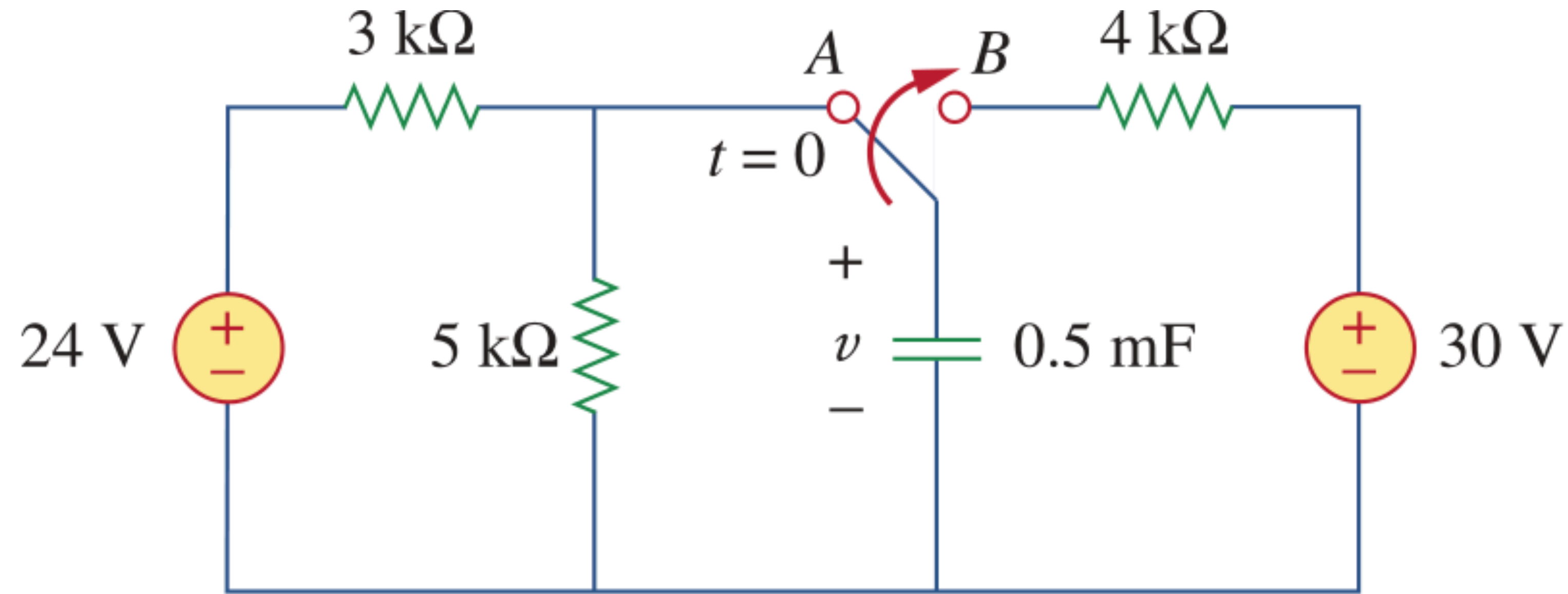

$$V_c(t) = V_\infty + (V_0 + V_\infty) e^{\frac{-t}{\tau}}$$


$$V_0 = 15V$$

$$\tau = 2s$$

$$V_\infty = 30V$$

Example 2- Step-Response in RC Circuits

- Determine $v(t)$

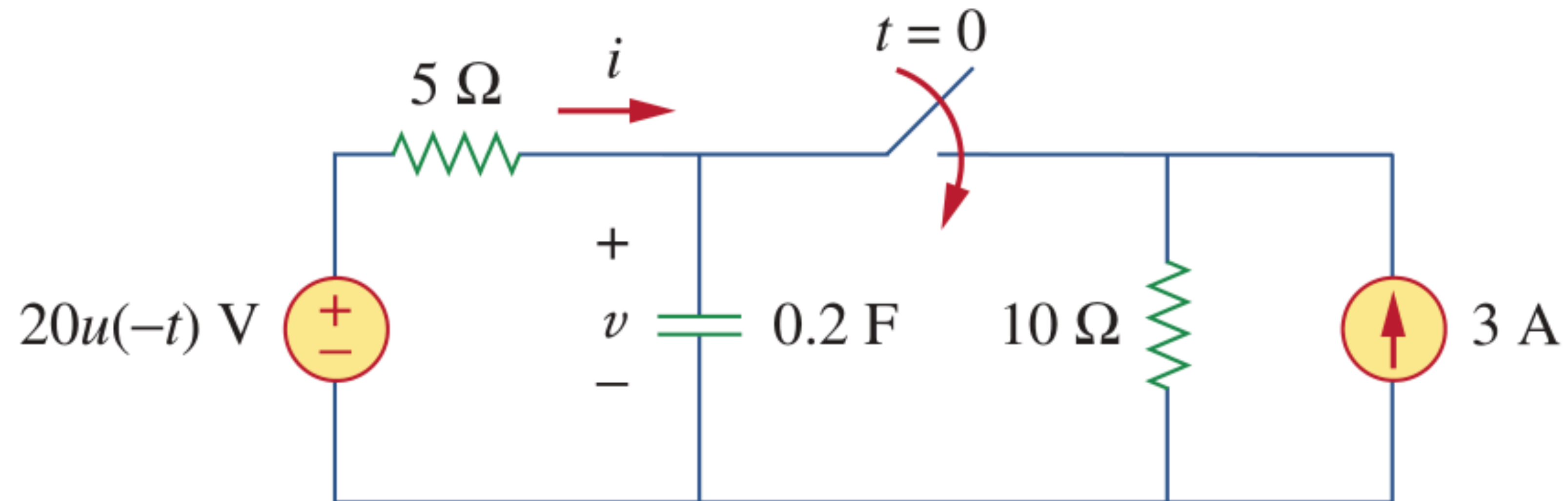

Unit Step Function

$$u(\tau) = \begin{cases} 1 & \text{if } \tau \geq 0 \\ 0 & \text{if } \tau < 0 \end{cases}$$

Draw $u(t)$, $u(t - 5)$, $u(-t)$

$$V_0 = 20V$$

$$\tau = 2/3 \text{ s}$$

$$V_\infty = 10V$$

$$V_c(t) = V_\infty + (V_0 + V_\infty) e^{\frac{-t}{\tau}}$$

