

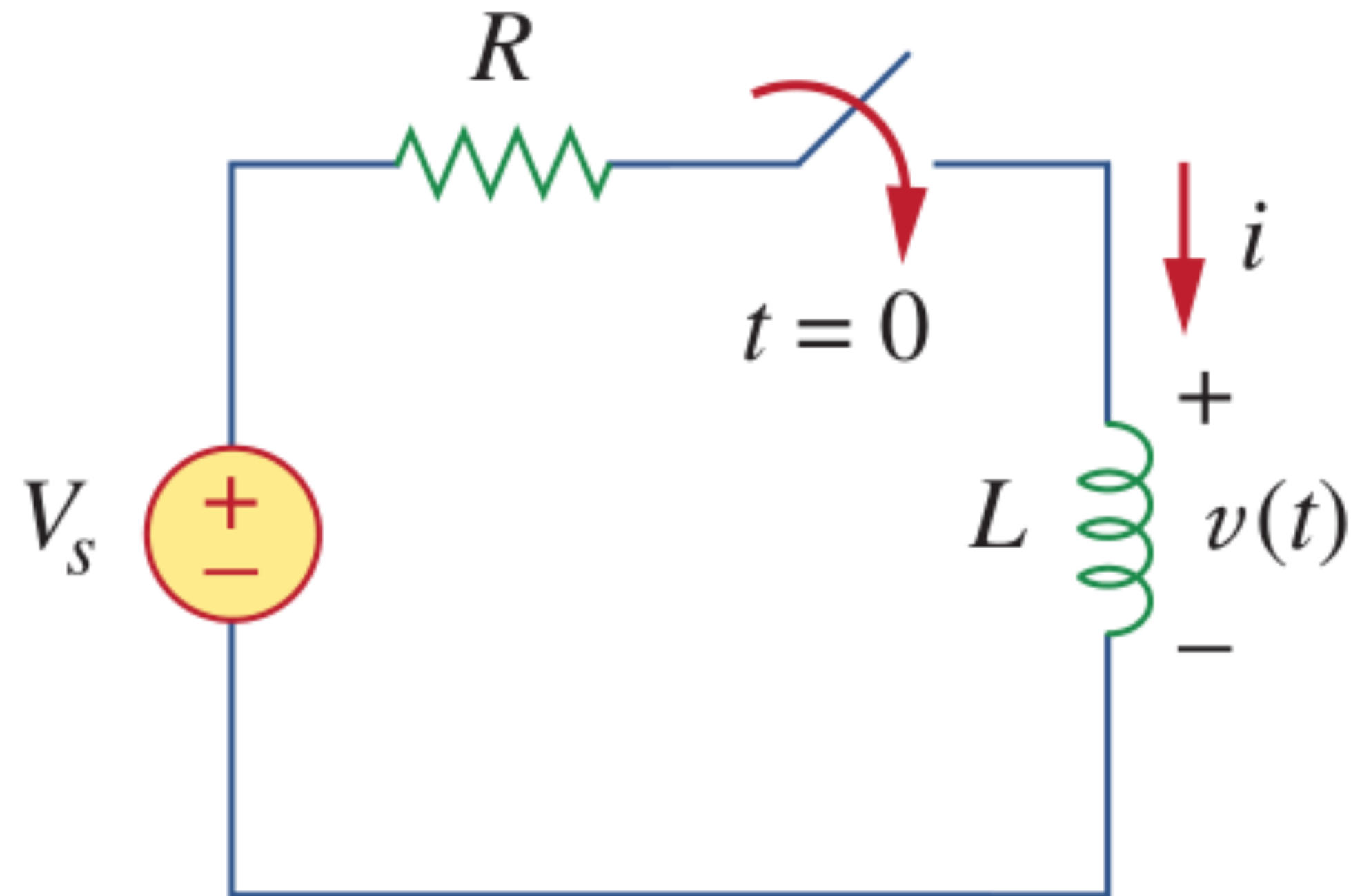

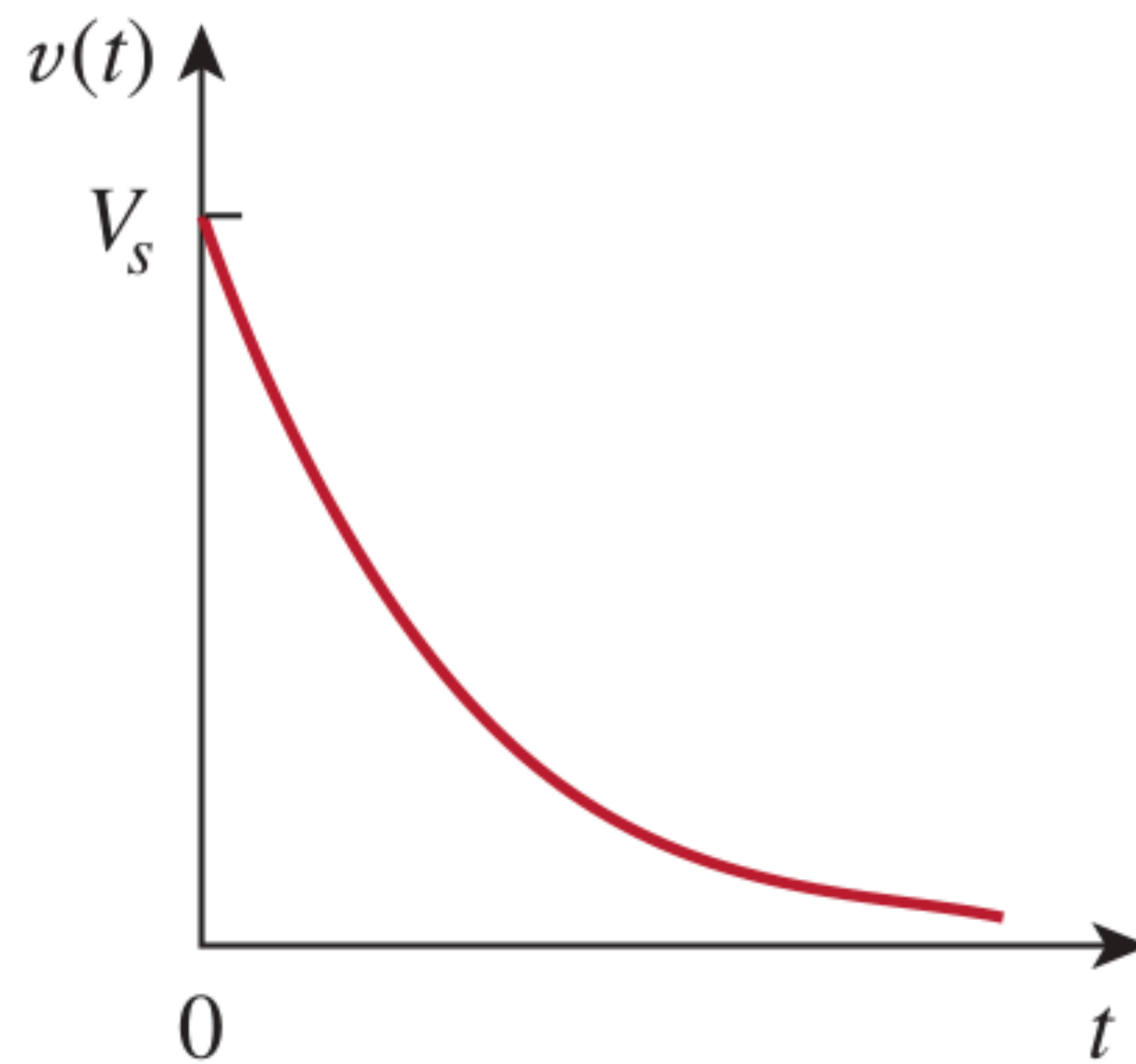
# Step Response - RL Circuits


- Assume that at  $t=0$ , the inductor current is equal to 0A



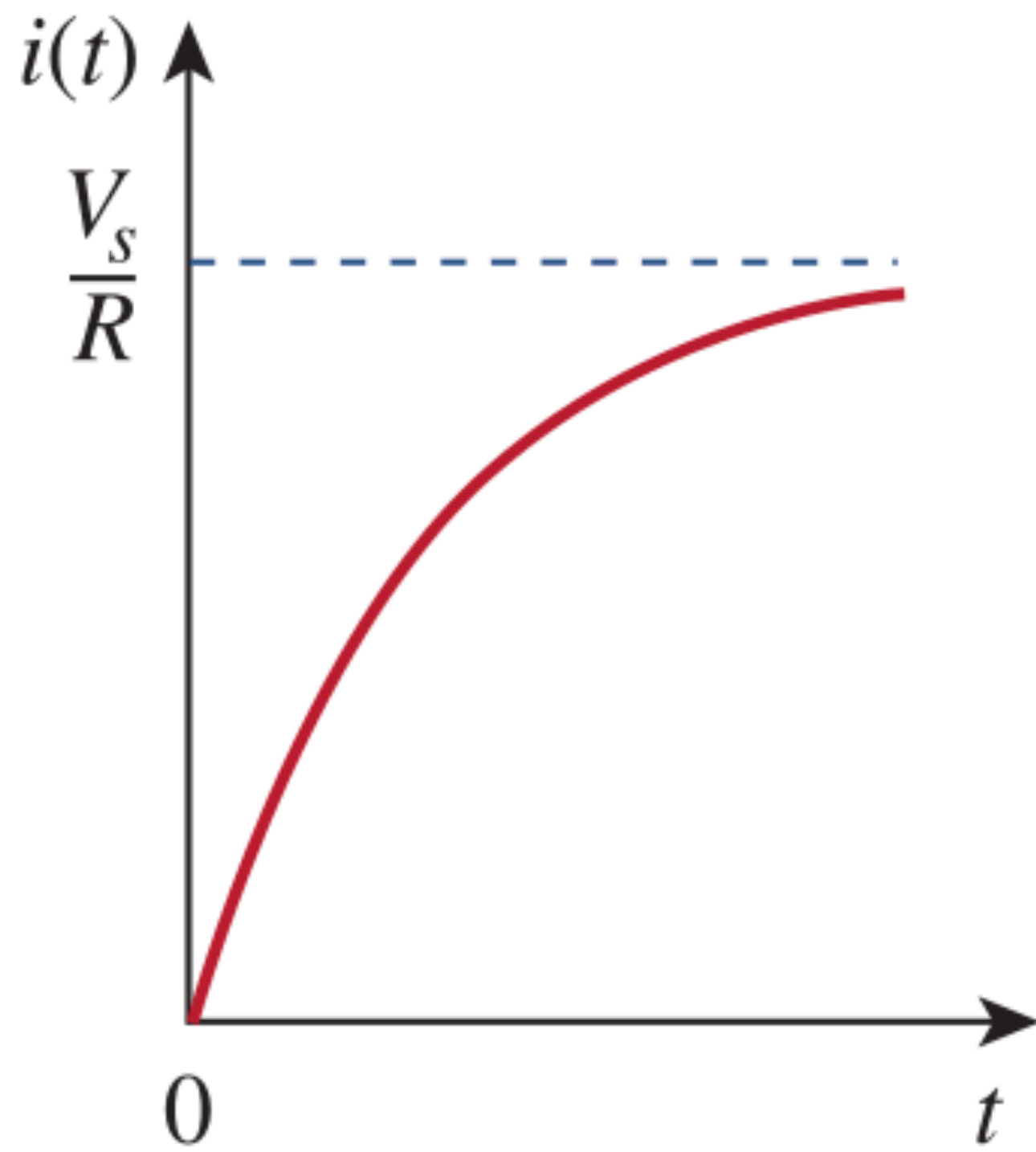
$$\begin{aligned}
 I_L(t) &= I_\infty \left(1 - e^{-t/\tau}\right) \\
 &= \frac{V_s}{R} \left(1 - e^{-t\frac{R}{L}}\right)
 \end{aligned}$$



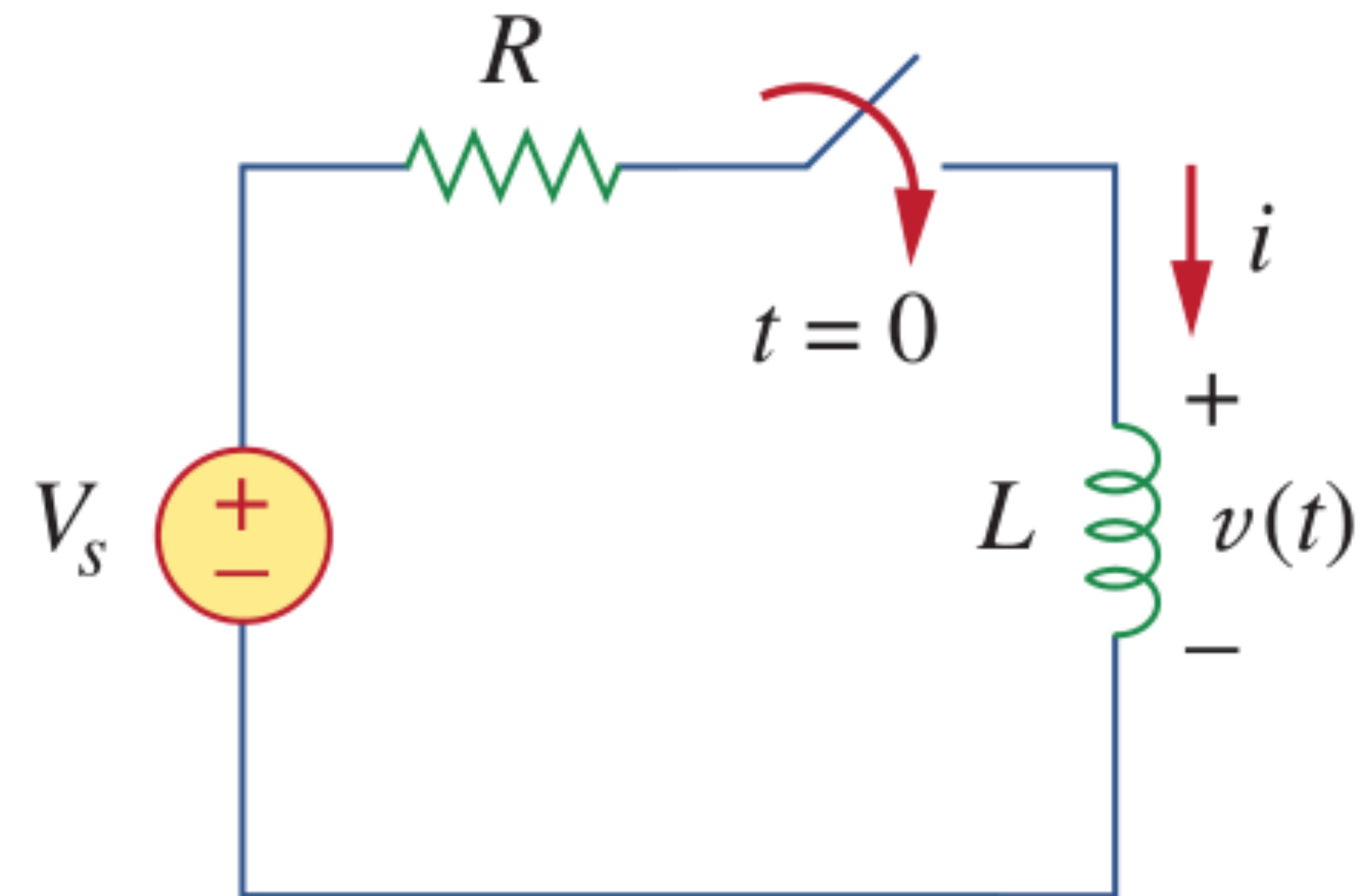
- Assume that at  $t=0$ , the inductor current is equal to  $I_0$




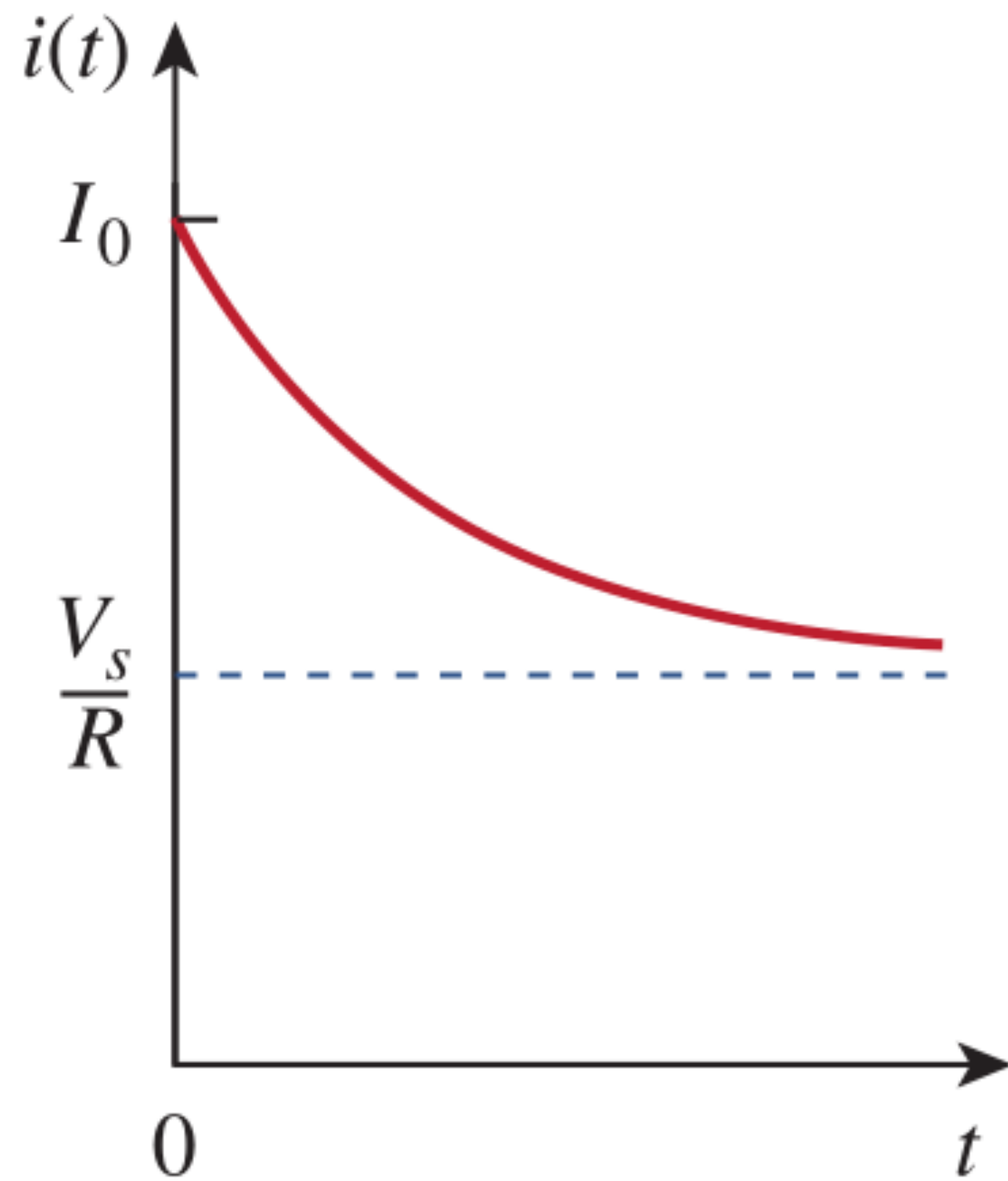

$$\begin{aligned} I_L(t) &= I_\infty + (I_0 - I_\infty)e^{-t/\tau} \\ &= \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R}\right)e^{-t\frac{R}{L}} \end{aligned}$$

- Determine  $i(t)$

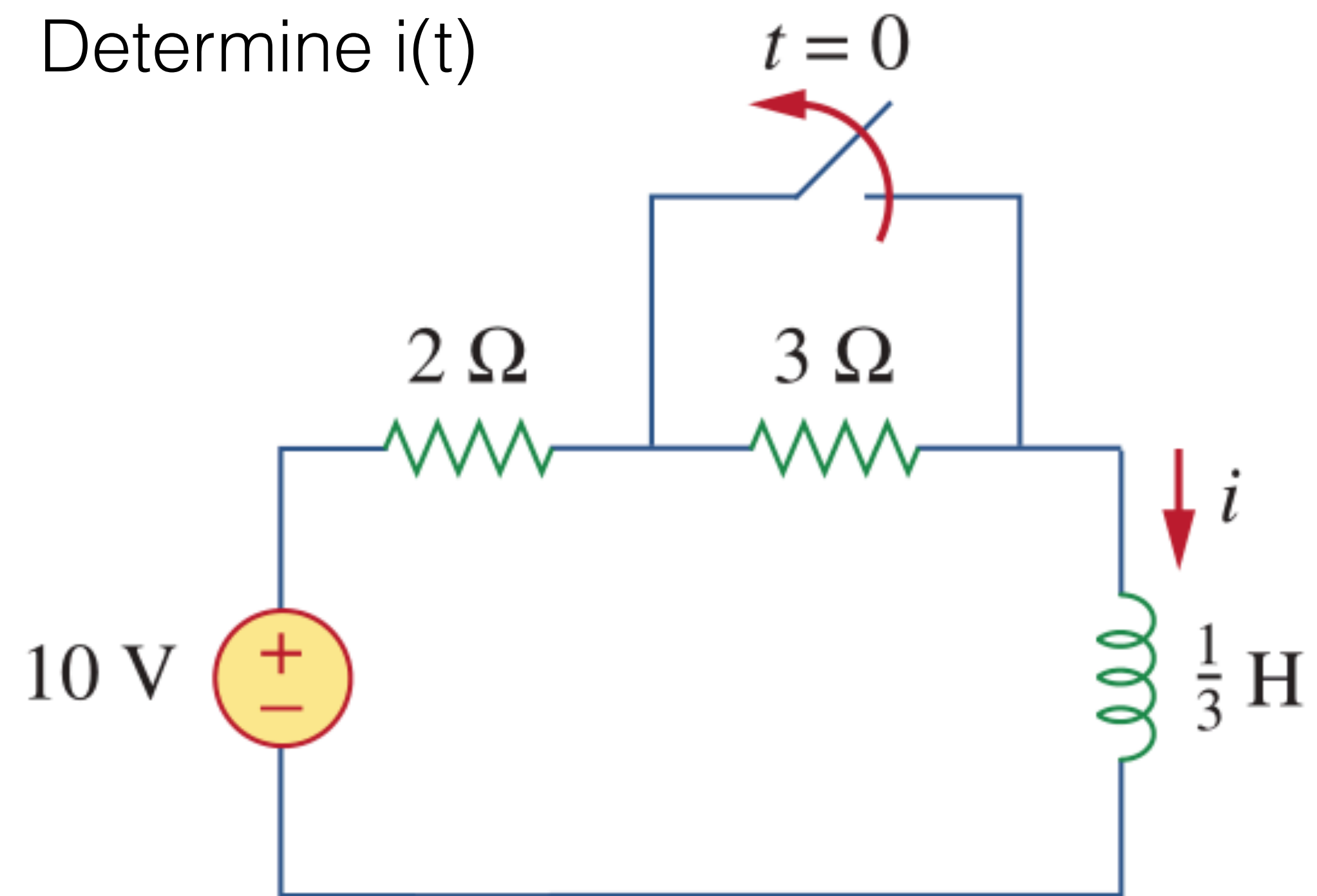

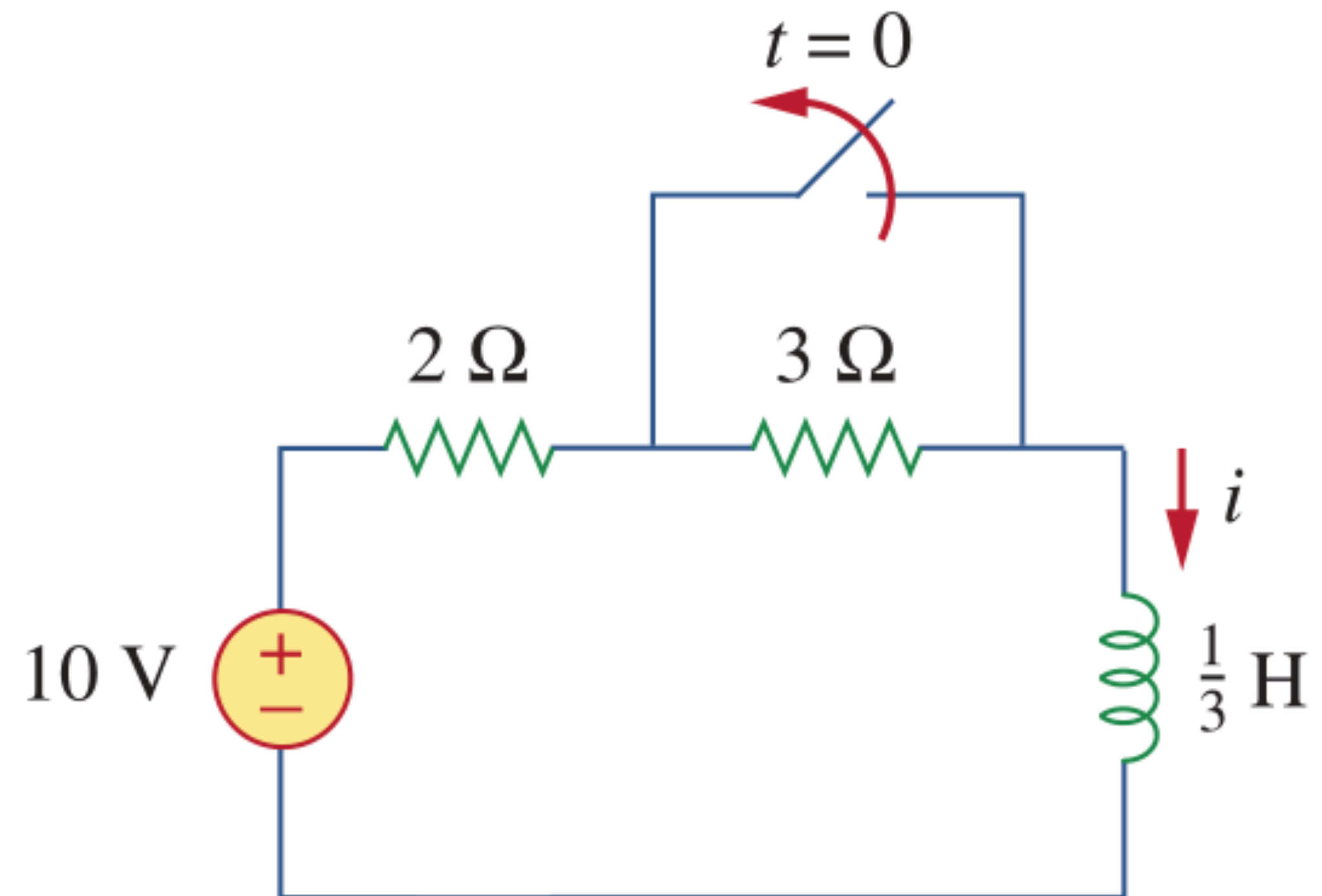


$$I_0 = 5A$$

$$\tau = 1/15s$$

$$V_\infty = 2A$$


$$I_L(t) = I_\infty + (I_0 - I_\infty)e^{-t/\tau}$$

- Determine  $i(t)$  given that  $i_0=0$

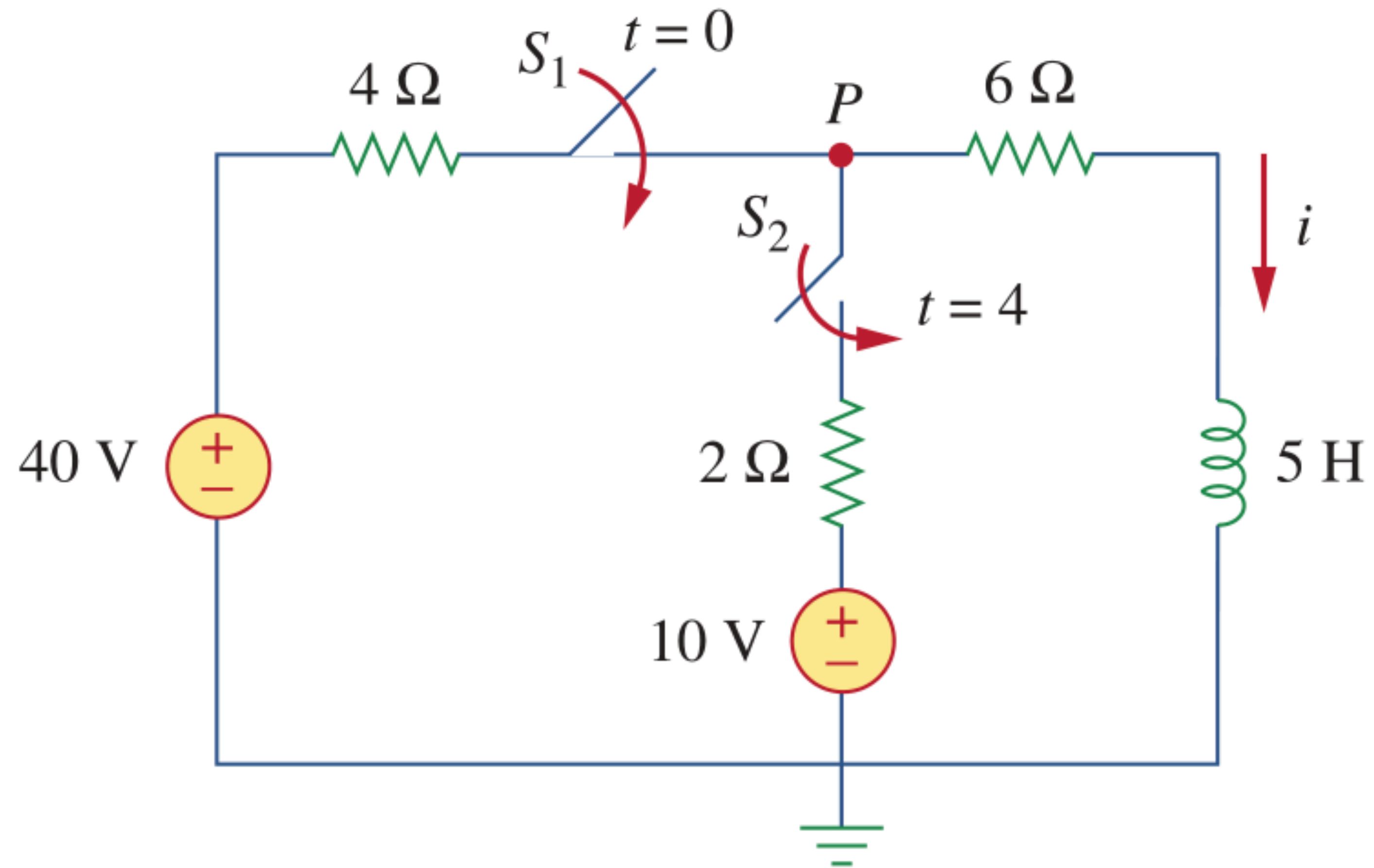


- Determine  $i(t)$  given that  $i_0=0$


$$i(t) = I_{\infty} (1 - e^{-t/\tau})$$

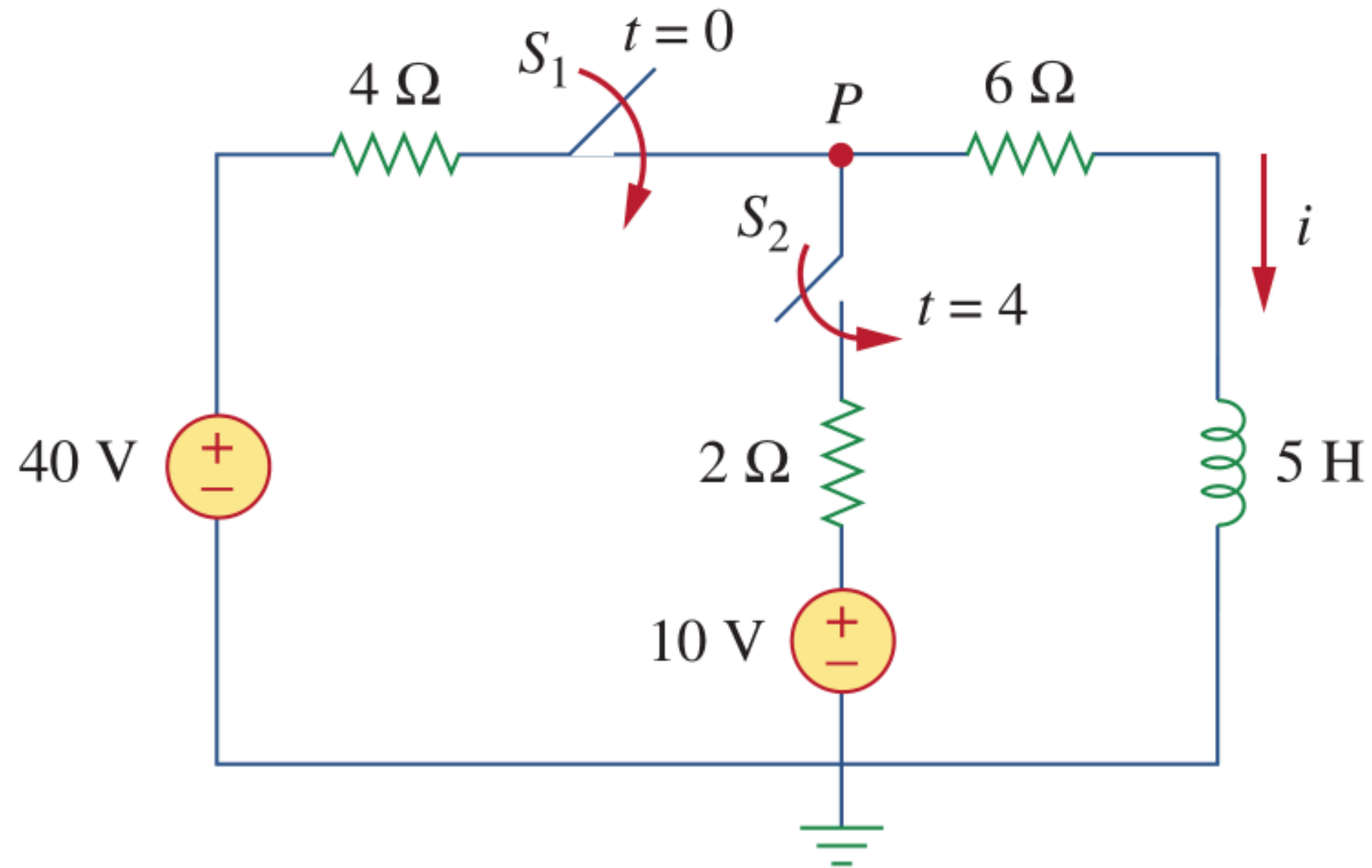



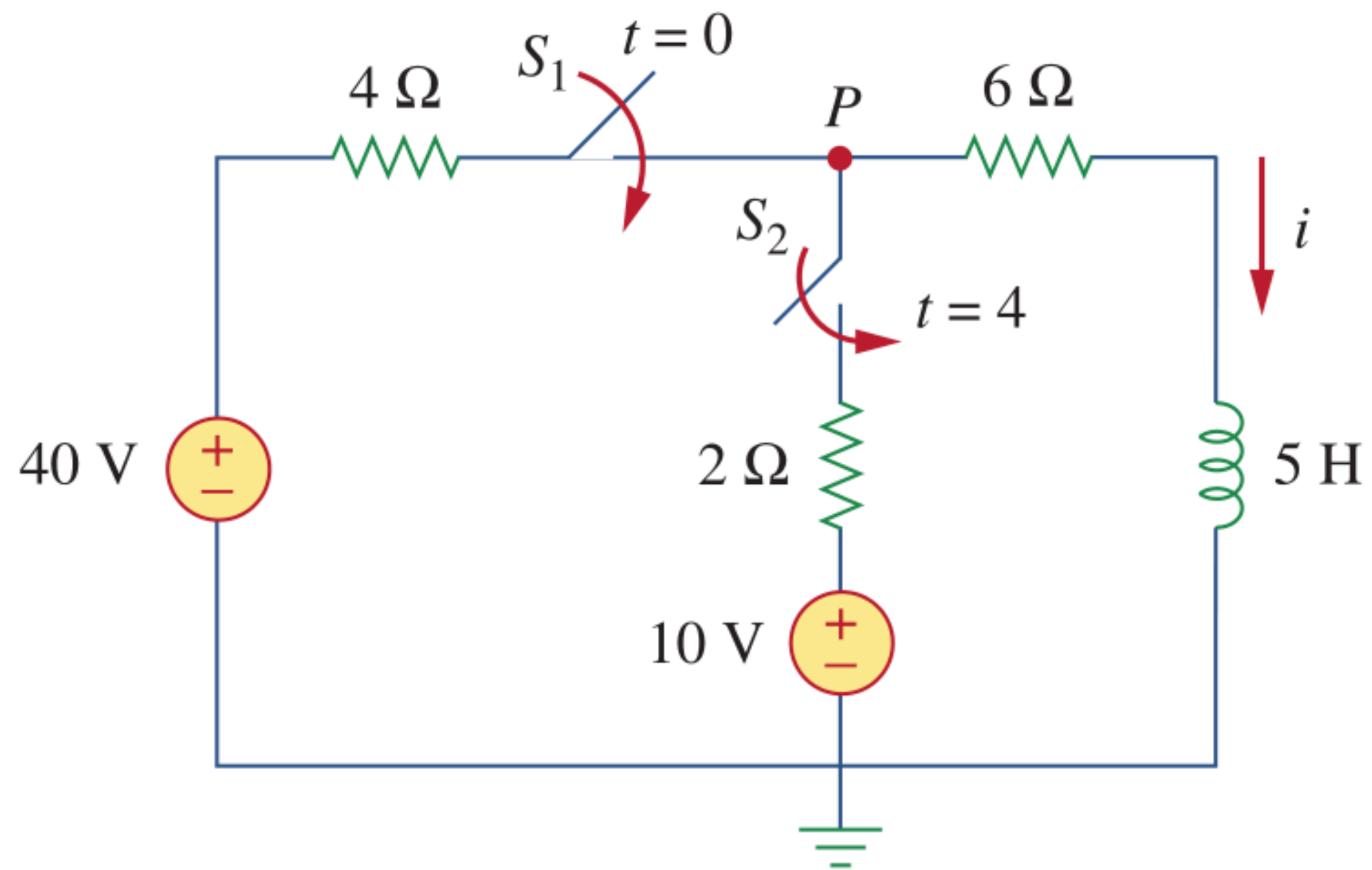
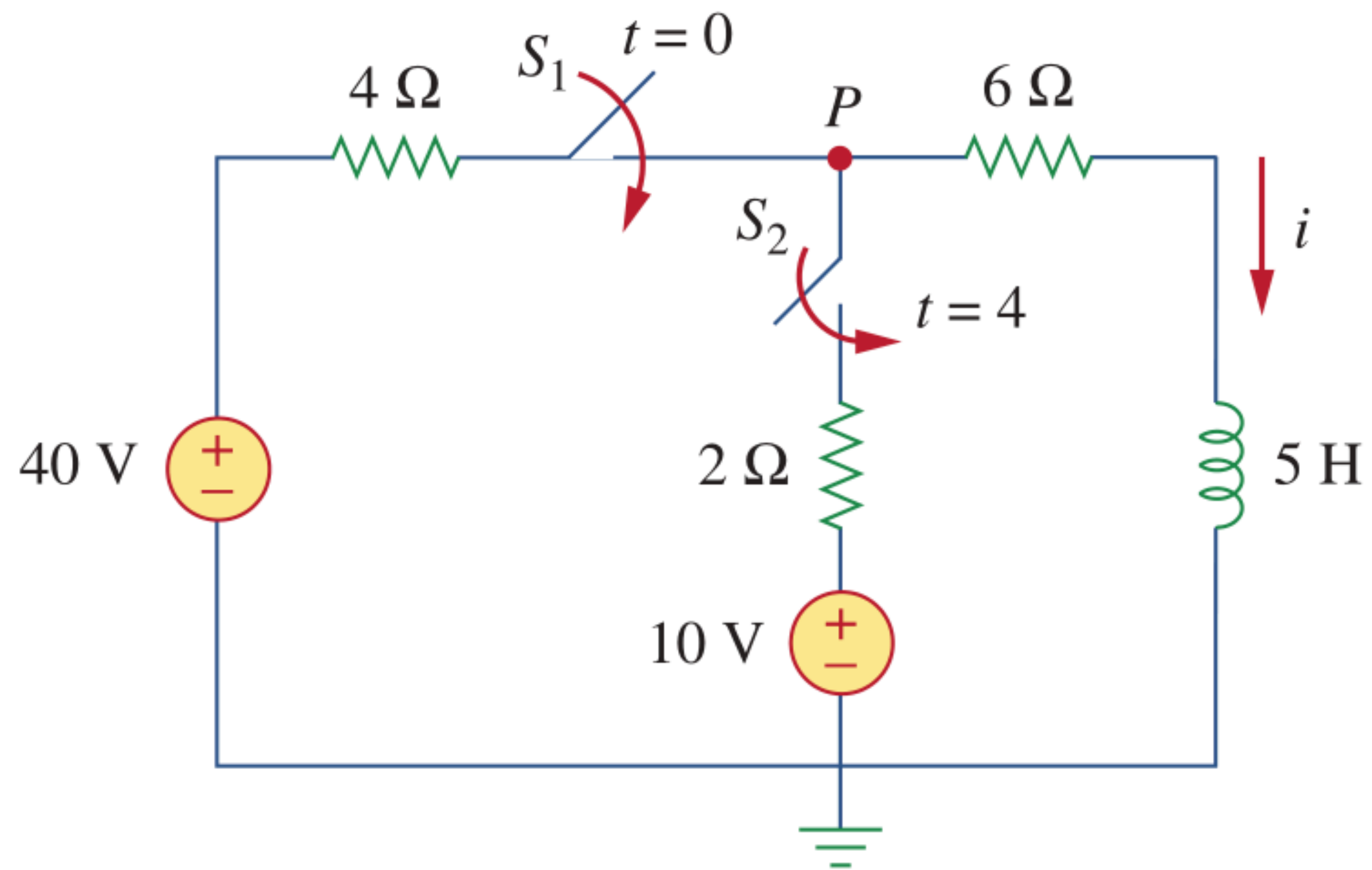
$$i(t) = 4A(1 - e^{-2t}) \text{ for } 4 > t > 0$$




$$i(t) = 4A(1 - e^{-2t}) \text{ for } 4 > t > 0$$

$$\hat{t} = t - 4$$

$$t \geq 4 \iff \hat{t} \geq 0$$
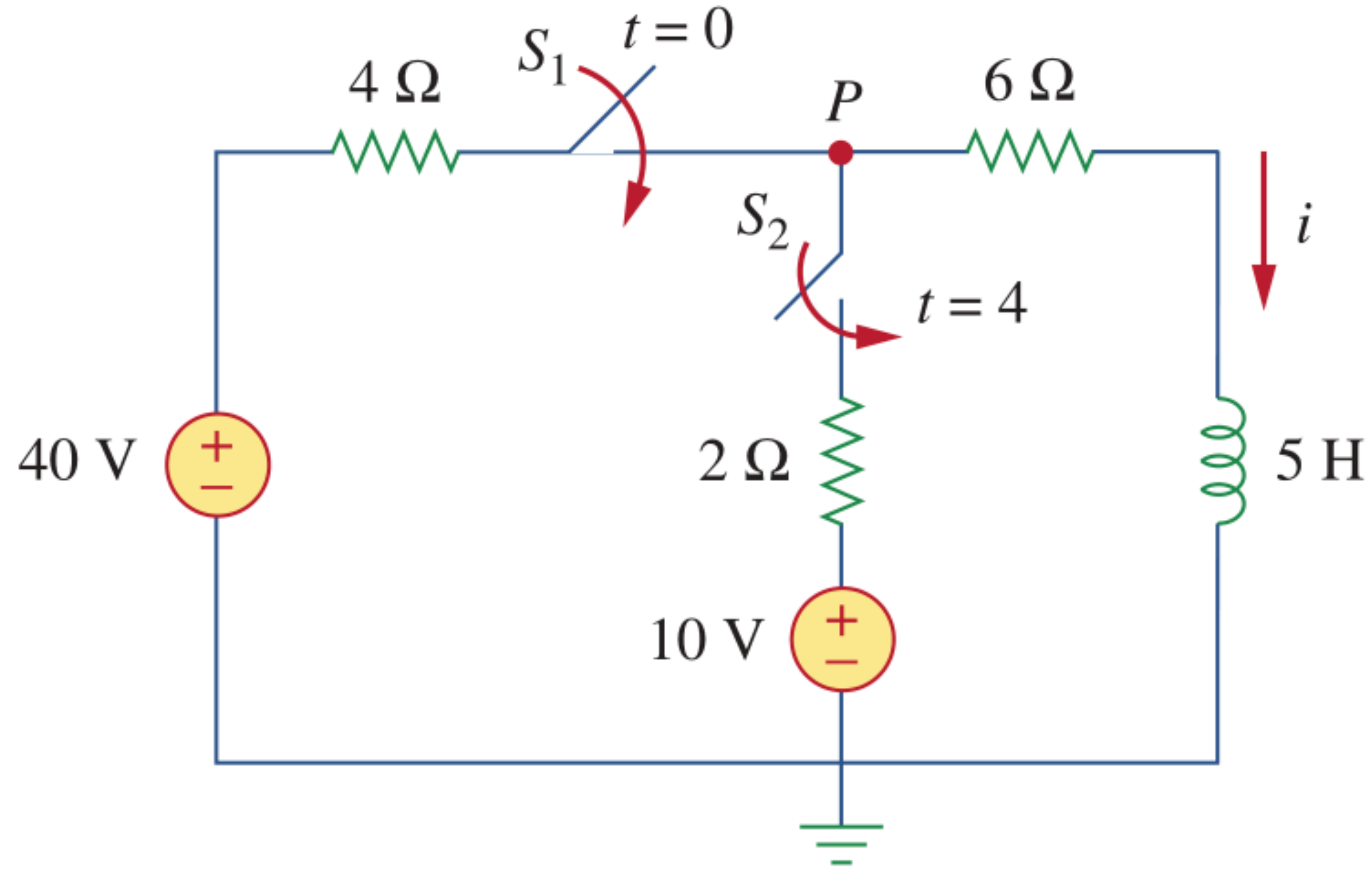
$$i(\hat{t}) = I_{\infty} + (I_{\hat{t}=0} - I_{\infty}) e^{-\hat{t}/\tau}$$



$$i(t) = 4(1 - e^{-2t})\text{A for } t \in [0, 4)$$

$$i(t) = (2.73 + 1.72e^{-1.5(t-4)})\text{ A for } t \in [4, \infty)$$